

Contents

1	DC Systems	1
1.1	Basic Quantities, Basic Laws	1
1.1.1	Electric Charge	1
1.1.2	Electric Current	1
1.1.3	Voltage and Potential	2
1.1.4	Ohm's Law	2
1.1.5	Resistance and Conductance	3
1.1.6	Temperature Dependence of Resistance	3
1.1.7	Inductance	4
1.1.8	Capacitance	4
1.1.9	Ideal Voltage Source	5
1.1.10	Ideal Current Source	5
1.1.11	Kirchhoff's Law	6
1.1.11.1	Kirchhoff's First Law (Current Law)	6
1.1.11.2	Kirchhoff's Second Law (Voltage Law)	6
1.1.12	Power and Energy	7
1.1.12.1	Energy and Power in a Resistor	7
1.1.12.2	Energy in an Inductor	8
1.1.12.3	Energy in a Capacitor	9
1.1.13	Efficiency	9
1.1.14	Maximum Power Transfer	10
1.2	Basic Circuits	11
1.2.1	Real Voltage and Current Sources	11
1.2.1.1	Real Voltage Source	11
1.2.1.2	Real Current Source	12
1.2.1.3	Voltage–Current Source Conversion	13
1.2.2	Circuit Elements in Series and Parallel	13
1.2.2.1	Series Combination of Resistors	13
1.2.2.2	Parallel Combination of Resistors	13
1.2.2.3	Series Combination of Conductances	14
1.2.2.4	Parallel Combination of Conductances	14
1.2.2.5	Series Combination of Inductances	15
1.2.2.6	Parallel Combination of Inductances	15
1.2.2.7	Series Combination of Capacitances	16
1.2.2.8	Parallel Combination of Capacitances	16
1.2.3	Star–Delta Transformation	17
1.2.4	Voltage and Current Divider	18
1.2.4.1	Voltage Divider	18
1.2.4.2	Current Divider	18
1.2.4.3	Capacitive and Inductive Dividers	19
1.2.5	RC and RL Combinations	19
1.2.5.1	Series Combination of R and C Driven by a Voltage Source	21
1.2.5.2	Series Combination of R and C Driven by a Current Source	21
1.2.5.3	Parallel Combination of R and C Driven by a Current Source	22
1.2.5.4	Parallel Combination of R and C Driven by a Voltage Source	22

1.2.5.5	Series Combination of R and L Driven by a Voltage Source	23
1.2.5.6	Series Combination of R and L Driven by a Current Source	23
1.2.5.7	Parallel Combination of R and L Driven by a Voltage Source	24
1.2.5.8	Parallel Combination of R and L Driven by a Current Source	24
1.2.6	RLC Combinations	25
1.2.6.1	Series Combination of R , L and C	26
1.3	Calculation Methods for Linear Circuits	29
1.3.1	Rules for Signs	29
1.3.2	Circuit Calculation with Mesh and Node Analysis	30
1.3.3	Superposition	31
1.3.4	Mesh Analysis	32
1.3.5	Node Analysis	33
1.3.6	Thévenin's and Norton's Theorem	33
1.3.6.1	Calculating a Load Current by Thévenin's Theorem	34
1.3.6.2	Calculating a Current Within a Network	36
1.4	Notation Index	37
1.5	Further Reading	38
2	Electric Fields	39
2.1	Electrostatic Fields	39
2.1.1	Coulomb's Law	39
2.1.2	Definition of Electric Field Strength	40
2.1.3	Voltage and Potential	41
2.1.4	Electrostatic Induction	42
2.1.5	Electric Displacement	43
2.1.6	Dielectrics	44
2.1.7	The Coulomb Integral	44
2.1.8	Gauss's Law of Electrostatics	45
2.1.9	Capacitance	46
2.1.10	Electrostatic Field at a Boundary	47
2.1.11	Overview: Fields and Capacitances of Different Geometric Configurations	48
2.1.12	Energy in an Electrostatic Field	49
2.1.13	Forces in an Electrostatic Field	50
2.1.13.1	Force on a Charge	50
2.1.13.2	Force at the Boundary	50
2.1.14	Overview: Characteristics of an Electrostatic Field	52
2.1.15	Relationship between the Electrostatic Field Quantities	53
2.2	Static Steady-State Current Flow	53
2.2.1	Voltage and Potential	53
2.2.2	Current	54
2.2.3	Electric Field Strength	54
2.2.4	Current Density	55
2.2.5	Resistivity and Conductivity	56
2.2.6	Resistance and Conductance	57
2.2.7	Kirchhoff's Laws	58
2.2.7.1	Kirchhoff's First Law (Current Law)	58
2.2.7.2	Kirchhoff's Second Law (Mesh Law)	59
2.2.8	Static Steady-State Current Flow at Boundaries	60

2.2.9	Overview: Fields and Resistances of Different Geometric Configurations	61
2.2.10	Power and Energy in Static Steady-State Current Flow	62
2.2.11	Overview: Characteristics of Static Steady-State Current Flow	63
2.2.12	Relationship Between Quantities in Static Steady-State Current Flow	64
2.3	Magnetic Fields	64
2.3.1	Force on a Moving Charge	65
2.3.2	Definition of Magnetic Flux Density	66
2.3.3	Biot–Savart’s Law	68
2.3.4	Magnetic Field Strength	69
2.3.5	Magnetic Flux	70
2.3.6	Magnetic Voltage and Ampere’s Law	71
2.3.7	Magnetic Resistance, Magnetic Conductance, Inductance	73
2.3.8	Materials in a Magnetic Field	74
2.3.8.1	Ferromagnetic Materials	75
2.3.9	Magnetic Fields at Boundaries	77
2.3.10	The Magnetic Circuit	78
2.3.11	Magnetic Circuit with a Permanent Magnet	80
2.3.12	Overview: Inductances of Different Geometric Configurations	82
2.3.13	Induction	83
2.3.13.1	Induction in a Moving Electrical Conductor	83
2.3.13.2	Faraday’s Law of Induction	84
2.3.13.3	Self-Induction	87
2.3.14	Mutual Induction	88
2.3.15	Transformer Principle	90
2.3.16	Energy in a Magnetic Field	90
2.3.16.1	Energy in a Magnetic Circuit with an Air Gap	91
2.3.17	Forces in a Magnetic Field	92
2.3.17.1	Force on a Current-Carrying Conductor	92
2.3.17.2	Force at the Boundaries	93
2.3.18	Overview: Characteristics of a Magnetic Field	94
2.3.19	Relationship between the Magnetic Field Quantities	95
2.4	Maxwell’s Equations	95
2.5	Notation Index	96
2.6	Further Reading	98

3 AC Systems 99

3.1	Mathematical Basics of AC	99
3.1.1	Sine and Cosine Functions	99
3.1.1.1	Addition of Sinusoidal Waveforms	100
3.1.2	Complex Numbers	101
3.1.2.1	Complex Arithmetic	102
3.1.2.2	Representation of Complex Numbers	103
3.1.2.3	Changing Between Different Representations	105
3.1.3	Complex Calculus	105
3.1.3.1	Complex Addition and Subtraction	105
3.1.3.2	Multiplication of Complex Numbers	106
3.1.4	Overview: Complex Number Arithmetic	107
3.1.5	The Complex Exponential Function	107
3.1.5.1	Exponential Function with Imaginary Exponents	108
3.1.5.2	Exponential Function with Complex Exponents	108
3.1.6	Trigonometric Functions with Complex Arguments	109
3.1.7	From Sinusoidal Waveforms to Phasors	109
3.1.7.1	Complex Magnitude	109

	3.1.7.2	Relationship Between Sinusoidal Waveforms and Phasors	110
	3.1.7.3	Addition and Subtraction of Phasors	111
3.2		Sinusoidal Waveforms	112
	3.2.1	Characteristics of Sinusoidal Waveforms	113
	3.2.2	Characteristics of Nonsinusoidal Waveforms	115
3.3		Complex Impedance and Admittance	116
	3.3.1	Impedance	116
	3.3.2	Complex Impedance of Passive Components	118
		3.3.2.1 Resistor	118
		3.3.2.2 Inductor	118
		3.3.2.3 Capacitor	118
	3.3.3	Admittance	119
	3.3.4	Complex Admittance of Passive Components	120
	3.3.5	Overview: Complex Impedance	121
3.4		Impedance of Passive Components	122
3.5		Combinations of Passive Components	123
	3.5.1	Series Combinations	123
		3.5.1.1 General Case	123
		3.5.1.2 Resistor and Inductor in Series	124
		3.5.1.3 Resistor and Capacitor in Series	125
		3.5.1.4 Resistor, Inductor and Capacitor in Series	126
	3.5.2	Parallel Combinations	128
		3.5.2.1 General Case	128
		3.5.2.2 Resistor and Inductor in Parallel	129
		3.5.2.3 Resistor and Capacitor in Parallel	130
		3.5.2.4 Resistor, Inductor and Capacitor in Parallel	132
	3.5.3	Overview of Series and Parallel Circuits	134
3.6		Network Transformations	135
	3.6.1	Transformation from Parallel to Series Circuits and Vice Versa	135
	3.6.2	Star–Delta (Wye–Delta) and Delta–Star (Delta–Wye) Transformations	137
	3.6.3	Circuit Duality	139
3.7		Simple Networks	140
	3.7.1	Complex Voltage and Current Division	140
	3.7.2	Loaded Complex Voltage Divider	142
	3.7.3	Impedance Matching	143
	3.7.4	Voltage Divider with Defined Input and Output Resistances	145
	3.7.5	Phase-Shifting Circuits	146
		3.7.5.1 RC Phase Shifter	146
		3.7.5.2 Alternative Phase-Shifting Circuits	148
	3.7.6	AC Bridges	149
		3.7.6.1 Balancing Condition	149
		3.7.6.2 Application: Measurement Technique	150
3.8		Power in AC Circuits	151
	3.8.1	Instantaneous Power	151
		3.8.1.1 Power in a Resistance	151
		3.8.1.2 Power in a Reactive Element	151
	3.8.2	Average Power	152
		3.8.2.1 Real Power	153
		3.8.2.2 Reactive Power	154
		3.8.2.3 Apparent Power	155
	3.8.3	Complex Power	155
	3.8.4	Overview: AC Power	156

3.8.5	Reactive Current Compensation	156
3.9	Three-Phase Supplies	158
3.9.1	Polyphase Systems	158
3.9.2	Three-Phase Systems	159
3.9.2.1	Properties of the Complex Operator a	160
3.9.3	Delta-Connected Generators	161
3.9.4	Star-Connected Generators	162
3.10	Overview: Symmetrical Three-Phase Systems	164
3.10.1	Power in a Three-Phase System	165
3.11	Notation Index	166
3.12	Further Reading	167
4	Current, Voltage and Power Measurement	169
4.1	Electrical Measuring Instruments	169
4.1.1	Moving-Coil Instrument	169
4.1.2	Ratiometer Moving-Coil Instrument	169
4.1.3	Electrodynamic Instrument	170
4.1.4	Moving-Iron Instrument	171
4.1.5	Other Instruments	171
4.1.6	Overview: Electrical Instruments	173
4.2	Measurement of DC Current and Voltage	174
4.2.1	Moving-Coil Instrument	174
4.2.2	Range Extension for Current Measurements	174
4.2.3	Range Extension for Voltage Measurements	175
4.2.4	Overload Protection	176
4.2.5	Systematic Measurement Errors in Current and Voltage Measurement	176
4.3	Measurement of AC Voltage and AC Current	177
4.3.1	Moving-Coil Instrument with Rectifier	177
4.3.2	Moving-Iron Instruments	179
4.3.3	Measurement Range Extension Using an Instrument Transformer	179
4.3.4	RMS Measurement	180
4.4	Power Measurement	181
4.4.1	Power Measurement in a DC Circuit	181
4.4.2	Power Measurement in an AC Circuit	182
4.4.2.1	Three-Voltmeter Method	183
4.4.2.2	Power Factor Measurement	184
4.4.3	Power Measurement in a Multiphase System	185
4.4.3.1	Measurement of the Real Power in a Multiphase System	185
4.4.3.2	Measurement of the Reactive Power in a Multiphase System	186
4.5	Measurement Errors	187
4.5.1	Systematic and Random Errors	187
4.5.2	Guaranteed Error Limits	188
4.6	Overview: Symbols on Measurement Instruments	188
4.7	Overview: Measurement Methods	190
4.8	Notation Index	190
4.9	Further Reading	191
5	Networks at Variable Frequency	192
5.1	Linear Systems	192
5.1.1	Transfer Function, Amplitude and Phase Response	192
5.2	Filters	194

5.2.1	Low-Pass Filter	195
5.2.2	High-Pass Filter	195
5.2.3	Bandpass Filter	196
5.2.4	Stop-Band Filter	197
5.2.5	All-Pass Filter	197
5.3	Simple Filters	197
5.3.1	Low-Pass Filter	197
5.3.1.1	Rise Time	198
5.3.2	Frequency Normalisation	199
5.3.2.1	Approximation of the Magnitude Response	200
5.3.3	High-Pass Filter	200
5.3.3.1	Approximation of the Magnitude Response	202
5.3.4	Higher-Order Filters	202
5.3.5	Bandpass Filter	204
5.3.6	Filter Realisation	206
5.4	Notation Index	206
5.5	Further Reading	207
6	Signals and Systems	208
6.1	Signals	208
6.1.1	Definitions	208
6.1.2	Symmetry Properties of Signals	209
6.2	Fourier Series	210
6.2.1	Trigonometric Form	210
6.2.1.1	Symmetry Properties	211
6.2.2	Amplitude–Phase Form	211
6.2.3	Exponential Form	212
6.2.3.1	Symmetry Properties	213
6.2.4	Overview: Fourier Series Representations	213
6.2.5	Useful Integrals for the Calculation of Fourier Coefficients	214
6.2.6	Useful Fourier Series	215
6.2.7	Application of the Fourier Series	217
6.2.7.1	Spectrum of a Rectangular Signal	217
6.2.7.2	Spectrum of a Sawtooth Signal	218
6.2.7.3	Spectrum of a Composite Signal	219
6.3	Systems	220
6.3.1	System Properties	220
6.3.1.1	Linear Systems	220
6.3.1.2	Causal Systems	221
6.3.1.3	Time-Invariant Systems	221
6.3.1.4	Stable Systems	222
6.3.1.5	LTI Systems	222
6.3.2	Elementary Signals	222
6.3.2.1	The Step Function	222
6.3.2.2	The Rectangular Pulse	222
6.3.2.3	The Triangular Pulse	223
6.3.2.4	The Gaussian Pulse	223
6.3.2.5	The Impulse Function (Delta Function)	224
6.3.3	Shifting and Scaling of Time Signals	225
6.3.4	System Responses	226
6.3.4.1	Impulse Response	226
6.3.4.2	Step Response	227
6.3.4.3	System Response to Arbitrary Input Signals	228
6.3.4.4	Rules of Convolution	228

	6.3.4.5	Transfer Function	230
	6.3.4.6	System Response Calculation in the Frequency Domain	230
6.3.5		Impulse and Step Response Calculation	231
	6.3.5.1	Normalisation of Circuits	231
	6.3.5.2	Impulse and Step Response of First-Order Systems	232
	6.3.5.3	Impulse and Step Response of Second-Order Systems	234
6.3.6		Ideal Systems	236
	6.3.6.1	Distortion-Free Systems	236
	6.3.6.2	Ideal Low-Pass Filter	238
	6.3.6.3	Ideal Bandpass Filter	240
6.4		Fourier Transforms	241
	6.4.1	Principle	241
	6.4.2	Definition	242
	6.4.3	Representation of the Fourier Transform	243
	6.4.3.1	Symmetry Properties	244
	6.4.4	Overview: Properties of the Fourier Transform	244
	6.4.5	Fourier Transforms of Elementary Signals	245
	6.4.5.1	Spectrum of the Delta Function	245
	6.4.5.2	Spectrum of the Signum and the Step Functions	246
	6.4.5.3	Spectrum of the Rectangular Pulse	247
	6.4.5.4	Spectrum of the Triangular Pulse	247
	6.4.5.5	Spectrum of the Gaussian Pulse	248
	6.4.5.6	Spectrum of Harmonic Functions	249
	6.4.6	Summary of Fourier Transforms	250
6.5		Nonlinear Systems	253
	6.5.1	Definition	253
	6.5.2	Characterisation of Nonlinear Systems	253
	6.5.2.1	Characteristic Equation	253
	6.5.2.2	Total Harmonic Distortion	254
	6.5.2.3	Signal-to-Intermodulation Ratio	255
6.6		Notation Index	258
6.7		Further Reading	259
7		Analogue Circuit Design	261
	7.1	Methods of Analysis	261
	7.1.1	Linearisation at the Operating Point	261
	7.1.2	AC Equivalent Circuit	262
	7.1.3	Input and Output Impedance	263
	7.1.3.1	Determination of the Input Impedance	263
	7.1.3.2	Determination of the Output Impedance	263
	7.1.3.3	Combination of Two-Terminal Networks	264
	7.1.4	Two-Port Networks	265
	7.1.4.1	Two-Port Network Equations	265
	7.1.4.2	Hybrid Parameters (<i>h</i> -Parameters)	265
	7.1.4.3	Admittance Parameters (<i>y</i> -Parameters)	266
	7.1.5	Block Diagrams	267
	7.1.5.1	Calculation Rules for Block Diagrams	268
	7.1.6	Bode Plot	269
	7.2	Silicon and Germanium Diodes	269
	7.2.1	Current-Voltage Characteristic of Si and Ge Diodes	270
	7.2.2	Temperature Dependency of the Threshold Voltage	270
	7.2.3	Dynamic Resistance (Differential Resistance)	271
	7.3	Small-Signal Amplifier with Bipolar Transistors	271
	7.3.1	Transistor Characteristics	272

7.3.1.1	Symbols, Voltages and Currents for Bipolar Transistors .	272
7.3.1.2	Output Characteristics	272
7.3.1.3	Transfer Characteristic	273
7.3.1.4	Input Characteristic	273
7.3.1.5	Static Current Gain β_{DC}	274
7.3.1.6	Differential Current Gain β	274
7.3.1.7	Transconductance g_m	275
7.3.1.8	Thermal Voltage Drift	275
7.3.1.9	Differential Input Resistance r_{BE}	275
7.3.1.10	Differential Output Resistance r_{CE}	275
7.3.1.11	Reverse Voltage-Transfer Ratio A_r	276
7.3.1.12	Unity Gain and Critical Frequencies	276
7.3.2	Equivalent Circuits	276
7.3.2.1	Static Equivalent Circuit	276
7.3.2.2	AC Equivalent Circuit	277
7.3.2.3	The Giacoletto Equivalent Circuit	278
7.3.3	Darlington Pair	278
7.3.3.1	Pseudo-Darlington Pair	279
7.3.4	Basic Circuits with Bipolar Transistors	280
7.3.5	Common-Emitter Circuit	280
7.3.5.1	Common-Emitter Circuit Two-Port Network Equations .	281
7.3.5.2	Common-Emitter AC Equivalent Circuit	282
7.3.5.3	Common-Emitter Circuit Input Impedance	283
7.3.5.4	Common-Emitter Circuit Output Impedance	284
7.3.5.5	Common-Emitter Circuit AC Voltage Gain	285
7.3.5.6	Operating Point Biasing	286
7.3.5.7	Operating Point Stabilisation	288
7.3.5.8	Load Line	290
7.3.5.9	Common-Emitter Circuit at High Frequencies	291
7.3.6	Common-Collector Circuit (Emitter Follower)	291
7.3.6.1	Common-Collector AC Equivalent Circuit	292
7.3.6.2	Common-Collector Circuit Input Impedance	293
7.3.6.3	Common-Collector Circuit Output Impedance	293
7.3.6.4	Common-Collector Circuit AC Current Gain	294
7.3.6.5	Common-Collector Circuit at High Frequencies	294
7.3.7	Common-Base Circuit	294
7.3.7.1	Common-Base AC Equivalent Circuit	295
7.3.7.2	Common-Base Circuit Input Impedance	295
7.3.7.3	Common-Base Circuit Output Impedance	295
7.3.7.4	Common-Base Circuit AC Voltage Gain	296
7.3.7.5	Common-Base Circuit at High Frequencies	296
7.3.8	Overview: Basic Bipolar Transistor Circuits	296
7.3.9	Bipolar Transistor Current Sources	296
7.3.10	Bipolar Transistor Differential Amplifier	298
7.3.10.1	Differential Mode Gain	300
7.3.10.2	Common-Mode Gain	301
7.3.10.3	Common-Mode Rejection Ratio	301
7.3.10.4	Differential Amplifier Input Impedance	302
7.3.10.5	Differential Amplifier Output Impedance	302
7.3.10.6	Offset Voltage of the Differential Amplifier	302
7.3.10.7	Differential Amplifier Offset Current	302
7.3.10.8	Input Offset Voltage Drift	302
7.3.10.9	Differential Amplifier Examples	303
7.3.11	Overview: Bipolar Transistor Differential Amplifiers	304

7.3.12	Current Mirror	304
7.3.12.1	Current Mirror Variations	305
7.4	Field-Effect Transistor Small-Signal Amplifiers	305
7.4.1	Transistor Characteristics and Ratings	305
7.4.1.1	Symbols, Voltages and Currents for Field-Effect Transistors	305
7.4.1.2	JFET Characteristic Curves	307
7.4.1.3	IGFET Characteristic Curves	307
7.4.1.4	Transconductance	308
7.4.1.5	Dynamic Output Resistance	309
7.4.1.6	Input Impedance	309
7.4.2	Equivalent Circuit	309
7.4.2.1	Equivalent Circuit for Low Frequencies	309
7.4.2.2	Equivalent Circuit for High Frequencies	310
7.4.2.3	Critical Frequency of Transconductance	310
7.4.3	Basic Circuits using Field-Effect Transistors	310
7.4.4	Common-Source Circuit	310
7.4.4.1	Common-Source Two-Port Parameters	311
7.4.4.2	AC Equivalent Circuit of the Common-Source Circuit	312
7.4.4.3	Input Impedance of the Common-Source Circuit	313
7.4.4.4	Output Impedance of the Common-Source Circuit	313
7.4.4.5	AC Voltage Gain	314
7.4.4.6	Operating-Point Biasing	314
7.4.4.7	Common-Drain Circuit, Source Follower	316
7.4.4.8	AC Equivalent Circuit of the common-drain Circuit	316
7.4.4.9	Input Impedance of the Common-Drain Circuit	317
7.4.4.10	Output Impedance of the Common-Drain Circuit	317
7.4.4.11	Voltage Gain of the Common-Drain Circuit	317
7.4.4.12	Common-Drain Circuit at High Frequencies	317
7.4.5	Common-Gate Circuit	317
7.4.5.1	Input Impedance of the Common-Gate Circuit	318
7.4.5.2	Output Impedance of the Common-Gate Circuit	318
7.4.5.3	Voltage Gain of the Common-Gate Circuit	318
7.4.6	Overview: Basic Circuits using Field-Effect Transistors	318
7.4.7	FET Current Source	319
7.4.8	Differential Amplifier with Field-Effect Transistors	319
7.4.8.1	Differential Mode Gain	320
7.4.8.2	Common-Mode Gain	320
7.4.8.3	Common-Mode Rejection Ratio	321
7.4.8.4	Input Impedance	321
7.4.8.5	Output Impedance	321
7.4.9	Overview: Differential Amplifier with FETs	321
7.4.10	Controllable Resistor FETs	321
7.5	Negative Feedback	322
7.5.1	Feedback Topologies	324
7.5.2	Influence of Negative Feedback on the Input and Output Impedance	326
7.5.2.1	Input and Output Impedance of the Four Kinds of Feedback	327
7.5.3	Influence of Negative Feedback on Frequency Response	327
7.5.4	Stability of Systems with Negative Feedback	328
7.6	Operational Amplifiers	329
7.6.1	Characteristics of the Operational Amplifier	330
7.6.1.1	Output Voltage Swing	330

7.6.1.2	Offset Voltage	330
7.6.1.3	Offset Voltage Drift	331
7.6.1.4	Common-Mode Input Swing	331
7.6.1.5	Differential Mode Gain	331
7.6.1.6	Common-Mode Gain	331
7.6.1.7	Common-Mode Rejection Ratio	332
7.6.1.8	Power Supply Rejection Ratio	332
7.6.1.9	Input Impedance	332
7.6.1.10	Output Impedance	332
7.6.1.11	Input Bias Current	332
7.6.1.12	Gain–Bandwidth Product (Unity Gain Frequency)	333
7.6.1.13	Critical Frequency	333
7.6.1.14	Slew Rate of the Output Voltage	333
7.6.1.15	Equivalent Circuit of the Operational Amplifier	333
7.6.2	Frequency Compensation	334
7.6.3	Comparators	335
7.6.4	Circuits with Operational Amplifiers	335
7.6.4.1	Impedance Converter (follower)	336
7.6.4.2	Noninverting Amplifier	336
7.6.4.3	Inverting Amplifier	337
7.6.4.4	Summing Amplifier	338
7.6.4.5	Difference Amplifier	339
7.6.4.6	Instrumentation Amplifier	340
7.6.4.7	Voltage-Controlled Current Source	341
7.6.4.8	Integrator	341
7.6.4.9	Differentiator	342
7.6.4.10	AC Voltage Amplifier with Single-Rail Supply	343
7.6.4.11	Voltage Setting with Defined Slew Rate	343
7.6.4.12	Schmitt Trigger	344
7.6.4.13	Triangle- and Square-Wave Generator	345
7.6.4.14	Multivibrator	346
7.6.4.15	Sawtooth Generator	346
7.6.4.16	Pulse-Width Modulator	346
7.7	Active Filters	348
7.7.1	Low-Pass Filters	349
7.7.1.1	Theory of Low-Pass Filters	349
7.7.1.2	Low-Pass Filter Calculations	356
7.7.1.3	Low-Pass Filter Circuits	357
7.7.2	High-Pass Filters	359
7.7.2.1	Theory of High-Pass Filters	359
7.7.2.2	High-Pass Filter Circuits	359
7.7.3	Bandpass Filters	361
7.7.3.1	Second-Order Bandpass Filter	361
7.7.3.2	Second-Order Bandpass Filter Circuit	362
7.7.3.3	Fourth- and Higher-Order Bandpass Filters	362
7.7.4	Universal Filter	363
7.7.5	Switched-Capacitor Filter	363
7.8	Oscillators	364
7.8.1	RC Oscillators	365
7.8.1.1	Phase-Shift Oscillator	365
7.8.1.2	Wien Bridge Oscillator	366
7.8.2	LC Tuned Oscillators	367
7.8.2.1	Meissner Oscillator	367
7.8.2.2	Hartley Oscillator	367

7.8.2.3	Colpitts Oscillator	368
7.8.3	Quartz/Crystal Oscillators	368
7.8.3.1	Pierce Oscillator	369
7.8.3.2	Quartz Oscillator with TTL Gates	370
7.8.4	Multivibrators	370
7.9	Heating and Cooling	370
7.9.1	Reliability and Lifetime	371
7.9.2	Temperature Calculation	373
7.9.2.1	Thermal Resistance	373
7.9.2.2	Thermal Capacity	374
7.9.2.3	Transient Thermal Impedance	375
7.10	Power Amplifiers	376
7.10.1	Emitter Follower	376
7.10.2	Complementary Emitter Follower in Class B Operation	379
7.10.3	Complementary Emitter Follower in Class C Operation	382
7.10.4	The Characteristic Curves of the Operation Classes	383
7.10.5	Complementary Emitter Follower in Class AB Operation	383
7.10.5.1	Biasing for Class AB Operation	384
7.10.5.2	Complementary Emitter Follower with Darlington Transistors	385
7.10.5.3	Current-Limiting Complementary Emitter Follower	386
7.10.6	Input Signal Injection to Power Amplifiers	386
7.10.6.1	Input Signal Injection using a Differential Amplifier	386
7.10.6.2	Input Signal Injection Using an Op-Amp	388
7.10.7	Switched-Mode Amplifiers	388
7.11	Notation Index	389
7.12	Further Reading	390

8 Digital Electronics **392**

8.1	Logic Algebra	392
8.1.1	Logic Variables and Logic Gates	392
8.1.1.1	Inversion	392
8.1.1.2	AND Function	392
8.1.1.3	OR Function	393
8.1.2	Logic Functions and their Symbols	393
8.1.2.1	Inverter (NOT)	394
8.1.2.2	AND Gate	394
8.1.2.3	OR Gate	394
8.1.2.4	NAND Gate	395
8.1.2.5	NOR Gate	395
8.1.2.6	XOR Gate, Exclusive OR	396
8.1.3	Logic Transformations	396
8.1.3.1	Commutative Laws	396
8.1.3.2	Associative Laws	397
8.1.3.3	Distributive Laws	397
8.1.3.4	Inversion Laws (DeMorgan's Rules)	398
8.1.4	Overview: Logic Transformations	398
8.1.5	Analysis of Logic Circuits	399
8.1.6	Sum of Products and Product of Sums	400
8.1.6.1	Sum of Products	400
8.1.6.2	Product of Sums	401
8.1.7	Systematic Reduction of a Logic Function	402
8.1.7.1	Karnaugh Map	402
8.1.7.2	The Quine–McCluskey Technique	406

8.1.8	Synthesis of Combinational Circuits	408
8.1.8.1	Implementation Using only NAND Gates	408
8.1.8.2	Implementation Using only NOR Gates	408
8.2	Electronic Realisation of Logic Circuits	409
8.2.1	Electrical Specification	409
8.2.1.1	Voltage Levels	409
8.2.1.2	Transfer Characteristic	409
8.2.1.3	Loading	410
8.2.1.4	Noise Margin	410
8.2.1.5	Propagation Delay Time	411
8.2.1.6	Rise Times	411
8.2.1.7	Power Loss	412
8.2.1.8	Minimum Slew Rate	412
8.2.1.9	Integration	412
8.2.2	Overview: Notation in Data Sheets	412
8.2.3	TTL Family	414
8.2.3.1	TTL Devices	414
8.2.3.2	Basic TTL Gate Circuit	416
8.2.4	CMOS Family	417
8.2.5	Comparison of TTL and CMOS	418
8.2.5.1	Other Logic Families	418
8.2.6	Special Circuit Variations	420
8.2.6.1	Outputs with Open Collector	420
8.2.6.2	Wired AND/OR	420
8.2.6.3	Tri-State Outputs	422
8.2.6.4	Schmitt Trigger Inputs	422
8.3	Combinational Circuits and Sequential Logic	423
8.3.1	Dependency Notation	423
8.3.1.1	Overview: Dependency Notation	425
8.3.2	Circuit Symbols for Combinational and Sequential Logic	425
8.4	Examples of Combinational Circuits	426
8.4.1	1-to- n Decoder	426
8.4.2	Multiplexer and Demultiplexer	426
8.4.2.1	Overview of Circuits	428
8.5	Latches and Flip-Flops	428
8.5.1	Flip-Flop Applications	428
8.5.2	SR Flip-Flop	429
8.5.2.1	SR Flip-Flop with Clock Input	430
8.5.3	D Flip-Flop	430
8.5.4	Master-Slave Flip-Flop	431
8.5.5	JK Flip-Flop	432
8.5.6	Flip-Flop Triggering	432
8.5.7	Notation for Flip-Flop Circuit Symbols	433
8.5.8	Overview: Flip-Flops	434
8.5.9	Overview: Edge-Triggered Flip-Flops	434
8.5.10	Synthesis of Edge-Triggered Flip-Flops	436
8.5.11	Overview: Flip-Flop Circuits	438
8.6	Memory	439
8.6.1	Memory Construction	439
8.6.2	Memory Access	440
8.6.3	Static and Dynamic RAMs	441
8.6.3.1	Variations of RAM	442
8.6.4	Read-Only Memory	443
8.6.5	Programmable Logic Devices	444

8.6.5.1	Principle of Operation	444
8.6.5.2	PLD Types	445
8.6.5.3	Output Circuits	446
8.7	Registers and Shift Registers	448
8.8	Counters	449
8.8.1	Asynchronous Counters	450
8.8.1.1	Binary Counter	450
8.8.1.2	Decimal Counter	450
8.8.1.3	Down Counter	453
8.8.1.4	Up/Down Counter	454
8.8.1.5	Programmable Counter	454
8.8.2	Synchronous Counters	455
8.8.2.1	Cascading Synchronous Counters	456
8.8.3	Overview: TTL and CMOS Counters	458
8.8.3.1	TTL Counters	459
8.8.3.2	CMOS Counters	459
8.9	Design and Synthesis of Sequential Logic	460
8.10	Further Reading	467
9	Power Supplies	469
9.1	Power Transformers	469
9.2	Rectification and Filtering	470
9.2.1	Different Rectifier Circuits	472
9.3	Analogue Voltage Stabilisation	473
9.3.1	Voltage Stabilisation with Zener Diode	473
9.3.2	Analogue Stabilisation with Transistor	474
9.3.3	Voltage Regulation	475
9.3.3.1	Integrated Voltage Regulators	475
9.4	Switched Mode Power Supplies	476
9.4.1	Single-Ended Converters, Secondary Switched SMPS	477
9.4.1.1	Buck Converter	477
9.4.1.2	Boost Converter	479
9.4.1.3	Buck-Boost Converter	481
9.4.2	Primary Switched SMPS	482
9.4.2.1	Flyback Converter	482
9.4.2.2	Single-Transistor Forward Converter	486
9.4.2.3	Push–Pull Converters	489
9.4.2.4	Resonant Converters	491
9.4.3	Overview: Switched-Mode Power Supplies	494
9.4.4	Control of Switched-Mode Power Supplies	496
9.4.4.1	Voltage-Mode Control	496
9.4.4.2	Current-Mode Control	497
9.4.4.3	Comparison: Voltage-Mode vs. Current-Mode Control	498
9.4.4.4	Design of the PI Controller	498
9.4.5	Design of Inductors and High-Frequency Transformers	499
9.4.5.1	Calculation of Inductors	499
9.4.5.2	Calculation of High-Frequency Transformers	500
9.4.6	Power Factor Control	504
9.4.6.1	Currents, Voltages and Power of the PFC	505
9.4.6.2	Controlling the PFC	506
9.4.7	Radio-Frequency Interference Suppression of Switched-Mode Power Supplies	507
9.4.7.1	Radio-Frequency Interference Radiation	507
9.4.7.2	Mains Input Conducted-Mode Interference	508

9.4.7.3	Suppression of Common-Mode Radio-Frequency Interference	509
9.4.7.4	Suppression of Differential-Mode Radio Frequency Interference	509
9.4.7.5	Complete Radio-Frequency Interference Filter	510
9.5	Notation Index	511
9.6	Further Reading	512
A	Mathematical Basics	513
A.1	Trigonometric Functions	513
A.1.1	Properties	513
A.1.2	Sums and Differences of Trigonometric Functions	514
A.1.3	Sums and Differences in the Argument	515
A.1.4	Multiples of the Argument	515
A.1.5	Weighted Sums of Trigonometric Functions	516
A.1.6	Products of Trigonometric Functions	516
A.1.7	Triple Products	516
A.1.8	Powers of Trigonometric Functions	517
A.1.9	Trigonometric Functions with Complex Arguments	517
A.2	Inverse Trigonometric Functions (Arc Functions)	517
A.3	Hyperbolic Functions	518
A.4	Differential Calculus	518
A.4.1	Basics of Differential Calculus	518
A.4.2	Derivatives of Elementary Functions	519
A.5	Integral Calculus	519
A.5.1	Basics of Integral Calculus	519
A.5.1.1	Integrals of Elementary Functions	520
A.5.2	Integrals Involving Trigonometric Functions	521
A.5.3	Integrals Involving Exponential Functions	523
A.5.4	Integrals Involving Inverse Trigonometric Functions	524
A.5.5	Definite Integrals	524
A.6	The Integral of the Standard Normal Distribution	527
B	Tables	530
B.1	The International System of Units (SI)	530
B.1.1	Decimal Prefixes	531
B.1.2	SI Units in Electrical Engineering	532
B.2	Naturally Occurring Constants	533
B.3	Symbols of the Greek Alphabet	533
B.4	Units and Definitions of Technical–Physical Quantities	534
B.5	Imperial and American Units	535
B.6	Other Units	537
B.7	Charge and Discharge Curves	540
B.8	IEC Standard Series	541
B.9	Resistor Colour Code	542
B.10	Parallel Combination of Resistors	543
B.11	Selecting Track Dimensions for Current Flow	544
B.12	American Wire Gauge	545
B.13	Dry Cell Batteries	546
B.14	Notation of Radio-Frequency Ranges	548
B.15	Ratios	549
B.15.1	Absolute Voltage Levels	549
B.15.1.1	Conversion of Power and Voltage Level Ratios	550
B.15.2	Relative Levels	551

B.16 V.24 Interface	552
B.17 Dual-Tone Multi-Frequency	553
B.18 ASCII Coding	554
B.19 Resolution and Coding for Analogue-to-Digital Converters	555
B.20 Chemical Elements	556
B.21 Materials	559
C Acronyms	561
D Circuit Symbols	595
Index	601