
Contents

Preface ix

Chapter 1. Photodiodes	1
1.1 The Photo Effect	1
1.2 The Photodiode Model	4
1.3 Photodiode Variations	7
1.3.1 PIN Photodiodes	7
1.3.2 Avalanche Photodiodes	9
1.4 Position-Sensing Photodiodes	10
1.4.1 The Basic Lateral Photodiode	11
1.4.2 The Lateral Photodiode Model	13
1.4.3 The Duo-Lateral Photodiode	15
1.4.4 The Tetra-Lateral Photodiode	17
References	19
Chapter 2. The Basic Amplifier	21
2.1 Linearity	21
2.2 Offset	24
2.2.1 Reducing Offset with a Compensation Resistor	24
2.2.2 Reducing Offset with a Feedback Tee	24
2.3 Bandwidth	28
References	30
Chapter 3. Bandwidth and Stability	31
3.1 The Inherent Response Limits	32
3.1.1 The Response Limit of Parasitic Capacitance	32
3.1.2 The Response Limit of Op Amp Bandwidth	33
3.2 The Phase Compensation Requirement	36
3.2.1 The <i>L-C</i> Tank Equivalent and Phase Compensation	36
3.2.2 Feedback Analysis of the Basic Circuit	38
3.3 Phase Compensation	42

3.3.1	The Basic Compensation	42
3.3.2	Phase Margin Analysis	43
3.3.3	Phase Margin Analysis of the Typical Case	45
3.3.4	Phase Margin Analysis of the Universal Case	47
3.3.5	Selecting the Phase Compensation Capacitor	49
3.4	The Bandwidth Advantage of the Current-to-Voltage Converter	50
3.5	Phase Compensation Alternatives	53
3.5.1	The Photodiode Amplifier's Second-Order Response	53
3.5.2	Translating the Second-Order Results to the Photodiode Amplifier	56
3.5.3	Selecting the Phase Compensation for Limited Peaking	57
3.5.4	Realizing the Precise Phase Compensation	59
	References	61
Chapter 4. Wideband Photodiode Amplifiers		63
4.1	Biasing the Photodiode	63
4.1.1	The Bias Effect	64
4.1.2	Photodiode Biasing with the Current-to-Voltage Converter	65
4.2	Bias Improvements	67
4.2.1	Filtering the Bias Voltage	67
4.2.2	Common-Mode Rejection of the Bias-Induced Errors	69
4.3	Bootstrapping the Photodiode	71
4.3.1	The Basic Bootstrap Photodiode Amplifier	71
4.3.2	Bandwidth Analysis of the Bootstrap Amplifier	74
4.3.3	Phase Compensating the Bootstrap Amplifier	74
4.4	Combining Bootstrapping with the Current-to-Voltage Converter	77
4.4.1	The Basic Combination and Its Requirements	77
4.4.2	A Practical Buffer Solution	80
4.4.3	Bandwidth Analysis of the Combination	83
	References	85
Chapter 5. Noise		87
5.1	General Noise Effects	87
5.1.1	Noise Densities and Noise Gains	88
5.1.2	Noise Gain Peaking	90
5.1.3	Total rms Output Noise	92
5.2	The Effect of Op Amp Input Noise Voltage	94
5.2.1	An Intuitive Derivation of the e_{noe} Noise Component	94
5.2.2	Simplifying the E_{noe} Analysis	95
5.2.3	The E_{noe} Components	97
5.3	Combining the Noise Effects	99
5.3.1	The Noise Analysis Summary	99
5.3.2	Identifying the Predominant Noise Effect	102
	References	106
Chapter 6. Noise Reduction		107
6.1	Noise Reduction with Feedback Capacitance C_f	108
6.1.1	The Noise Gain Reduction of C_f	108
6.1.2	Noise Analysis for the C_f Case	110

6.2	Noise Bandwidth versus Signal Bandwidth	112
6.3	Noise Reduction with a Composite Amplifier	112
6.3.1	The Noise Bandwidth Reduction of the Composite Amplifier	112
6.3.2	The Noise Gain Reduction of the Composite Amplifier	115
6.3.3	Optimizing the Composite Noise-versus-Bandwidth Compromise	117
6.3.4	Noise Analysis for the Composite Case	118
6.3.5	A Comparison with the Active Filter Alternative	120
6.4	Noise Reduction with Decoupling Phase Compensation	121
6.4.1	The Noise Gain Reduction of the Decoupling	122
6.4.2	Optimizing the Decoupling Noise-versus-Bandwidth Compromise	123
6.4.3	Noise Analysis for the Decoupling Case	126
	References	128
Chapter 7. High-Gain Photodiode Amplifiers		129
7.1	Using a Feedback Tee Network	130
7.1.1	The Gain and Noise Produced by a Feedback Tee	130
7.1.2	Optimizing the Tee's Noise Voltage Response	134
7.1.3	Optimizing the Tee's Resistance Noise Response	135
7.1.4	Noise Analysis for the Tee Case	138
7.2	Adding a Voltage Amplifier	140
7.2.1	Optimizing the Two-Amplifier Bandwidth-versus-Noise Compromise	141
7.2.2	Designing for the Bandwidth-versus-Noise Optimum	144
7.2.3	Noise Analysis for the Two-Amplifier Case	146
7.3	Adding Voltage Gain	150
7.3.1	Voltage Gain Alternatives	150
7.3.2	Optimizing the Single-Amplifier Bandwidth-versus-Noise Compromise	152
7.3.3	Noise Analysis for the Single-Amplifier Case	155
7.4	Adding Current Gain	157
7.4.1	Current Gain Alternatives	157
7.4.2	Optimizing the Current-Gain Bandwidth-versus-Noise Compromise	161
7.4.3	Noise Analysis for the Current Gain Case	163
	References	164
Chapter 8. Reducing Power-Supply Noise Coupling		165
8.1	The Power-Supply Bypass Requirement	166
8.1.1	The Noise-Coupling Mechanism	167
8.1.2	The Noise-Coupling Frequency Response	168
8.1.3	Power-Supply Coupling and Frequency Stability	170
8.1.4	The Oscillation Condition	172
8.2	Selecting the Primary Bypass Capacitor	173
8.2.1	Bypass Resonances	174
8.2.2	An Intuitive Evaluation of Bypass Resonance	176
8.2.3	The Bypass Selection	177
8.3	Selecting a Secondary Bypass Capacitor	179
8.3.1	Bypass Capacitor Self-Resonance	179

8.3.2	Dual Bypass Capacitors	182
8.3.3	Dual Bypass Selection	183
8.4	Bypass Alternatives	185
8.4.1	Detuning the Dual Bypass Resonance	186
8.4.2	Selecting the Detuning Resistance	188
8.5	Power-Supply Decoupling	191
8.5.1	Decoupling Alternatives	191
8.5.2	Selecting the Decoupling Components	195
	References	196
Chapter 9. Reducing External Noise Effects		197
9.1	Reducing Electrostatic Coupling	198
9.1.1	Electrostatic Shielding	198
9.1.2	The Differential-Input Current-to-Voltage Converter	199
9.1.3	Other Noise Effects of the Differential-Input Connection	202
9.1.4	An Alternate Differential-Input Photodiode Amplifier	207
9.1.5	Other Noise Effects of the Differential-Input Alternative	209
9.2	Reducing Magnetic and RFI Coupling	210
9.2.1	Magnetic Shielding	210
9.2.2	Circuit Reductions of Magnetic Coupling	212
9.3	Reducing Multiple Coupled-Noise Effects	216
9.4	Minimizing Magnetic Field Generation	216
	References	219
Chapter 10. Position-Sensing Photodiode Amplifiers		221
10.1	Direct-Displacement Monitor Amplifiers	222
10.1.1	Single-Axis Monitoring with a Differential-Photodiode Amplifier	222
10.1.2	Noise Reduction with the Differential-Photodiode Amplifier	224
10.1.3	Connecting the Photodiodes Differentially	225
10.1.4	An Alternate Differential-Photodiode Connection	227
10.1.5	Two-Axis Monitoring	229
10.2	Normalized Monitor Amplifiers	231
10.2.1	Normalizing the Differential-Photodiode Amplifier	232
10.2.2	Easing the Normalization	234
10.2.3	Simplifying the Normalized Differential-Photodiode Amplifier	237
10.3	A Digital Alternative to Normalization	239
10.3.1	Processing the Array Signals	239
10.3.2	Defining the Logic Output Levels	241
	References	243
Glossary		245
Index		249