

---

# Contents

Editor.....	ix
Contributors.....	xi

## **PART I CMOS Technology at the Nanoscale**

<b>Chapter 1</b> CMOS: An Emerging Technology System Driver .....	3
<i>Paul Rousseau</i>	
<b>Chapter 2</b> CMOS Manufacturability .....	11
<i>Artur Balasinski</i>	
<b>Chapter 3</b> Variability in Deeply Scaled CMOS .....	25
<i>Liang-Teck Pang and Borivoje Nikolić</i>	
<b>Chapter 4</b> Wafer-Level Three-Dimensional Integration for Advanced CMOS Systems .....	39
<i>Ronald J. Gutmann and Jian-Qiang Lu</i>	
<b>Chapter 5</b> CMOS SOI Memory Design Technology .....	53
<i>Kazutami Arimoto and Fukashi Morishita</i>	
<b>Chapter 6</b> SiGe Technology.....	75
<i>Marco Racanelli</i>	

## **PART II Emerging Design Techniques**

<b>Chapter 7</b> Offset, Flicker Noise, and Ways to Deal with Them .....	95
<i>Hanspeter Schmid</i>	
<b>Chapter 8</b> Design of Wideband Amplifiers in CMOS .....	117
<i>David J. Allstot, Sudip Shekhar, and Jeffrey S. Walling</i>	

<b>Chapter 9</b>	CMOS Active Transformers and Their Applications .....	135
	<i>Fei Yuan</i>	
<b>Chapter 10</b>	High-Performance Leakage/Variation-Tolerant Circuit Technologies for 45 nm and Below .....	149
	<i>Amit Agarwal and Ram Krishnamurthy</i>	
<b>Chapter 11</b>	Soliton and Nonlinear Wave Electronics .....	159
	<i>David S. Ricketts, Xiaofeng Li, and Donhee Ham</i>	

## **PART III Mixed-Signal CMOS Circuits**

<b>Chapter 12</b>	Current Steering Digital-to-Analog Converters .....	187
	<i>Douglas A. Mercer</i>	
<b>Chapter 13</b>	High-Speed, Low-Power CMOS A/D Converter for Software Radio .....	213
	<i>James W. Haslett and Abdel-Fattah S. Yousif</i>	
<b>Chapter 14</b>	Energy-Efficient ADC Topology Enabled with Asynchronous Techniques .....	225
	<i>Shuo-Wei Mike Chen</i>	
<b>Chapter 15</b>	High-Frequency Filters for Data Communication Applications .....	245
	<i>Manisha Gambhir, Vijay Dhanasekaran, Jose Silva-Martinez, and Edgar Sánchez-Sinencio</i>	
<b>Chapter 16</b>	Continuous Time $\Sigma\Delta$ Modulators .....	267
	<i>Robert Sobot</i>	

## **PART IV Circuits for Communications**

<b>Chapter 17</b>	Low-Voltage Nanometer-Scale CMOS RF Front-End Block Design Employing Magnetic Feedback Techniques .....	289
	<i>Yannis Papananos, Georgios Vitzilaios, and Gerasimos Theodoratos</i>	
<b>Chapter 18</b>	InGaP-HBT Power Amplifiers .....	319
	<i>Kazuya Yamamoto</i>	

<b>Chapter 19</b>	$\Delta\Sigma$ Digital-RF Modulation for Adaptive Wideband Systems .....	343
	<i>Albert Jerng and Charles G. Sodini</i>	
<b>Chapter 20</b>	Mitigation of CMOS Device Variability in Digital RF Processor .....	363
	<i>Khurram Waheed and Robert Bogdan Staszewski</i>	
<b>Chapter 21</b>	Front-End Circuits for Multi-Gb/s Chip-to-Chip Links .....	383
	<i>Anthony Chan Carusone</i>	
<b>Chapter 22</b>	Clock and Data Recovery Circuits .....	401
	<i>Jafar Savoj</i>	

## **PART V** *Circuits for Imaging and Sensing*

<b>Chapter 23</b>	Low Power CMOS Imager Circuits .....	421
	<i>Alexander Fish and Orly Yadid-Pecht</i>	
<b>Chapter 24</b>	CMOS Imager Array Design, Operation, and Trends .....	449
	<i>Mark Jaffe, John Ellis-Monaghan, and Jim Adkisson</i>	
<b>Chapter 25</b>	Wide Dynamic Range CMOS Cameras .....	467
	<i>Steve Collins, Bhaskar Choubey, Hsiu-Yu Cheng, and Stephen Otim</i>	
<b>Chapter 26</b>	CMOS Focal Plane Spatially Oversampling Computational Image Sensor .....	485
	<i>Ashkan Olyaei and Roman Genov</i>	
<b>Chapter 27</b>	Unified Computer Arithmetic for Handheld GPUs .....	503
	<i>Byeong-Gyu Nam, Hyejung Kim, and Hoi-Jun Yoo</i>	
<b>Chapter 28</b>	Sense Circuits for Integrated Sensors .....	525
	<i>Sitaraman V. Iyer and Hasnain Lakdawala</i>	
<b>Chapter 29</b>	Detector Interface Circuits for X-Ray Imaging .....	539
	<i>Pawel Grybos</i>	

<b>Chapter 30</b>	CMOS Systems and Interfaces for Microgyroscopes.....	565
	<i>Ajit Sharma, Mohammad F. Zaman, and Farrokh Ayazi</i>	
<b>Chapter 31</b>	Analog Front End for a Micromachined Probe Storage Device.....	587
	<i>Christoph Hagleitner, Tony Bonaccio, Hugo Rothuizen, Jan Lienemann, Dorothea Wiesmann, Giovanni Cherubini, Jan G. Korvink, and Evangelos Eleftheriou</i>	
<b>Index</b>	.....	609