

# Contents

<i>Preface to the second edition</i>	page xi
<i>Preface to the first edition</i>	xiii
<b>1 Principles of amplifiers</b>	<b>1</b>
1.1 Introduction	1
1.2 Coupling between voltage amplifiers	3
1.3 Worked example	5
1.4 Logarithmic expression for gain: the decibel	6
1.5 Coupling between current amplifiers	8
1.6 Loading of a source for maximum power output	9
1.7 Frequency characteristics of coupling circuits and amplifiers	11
1.8 Coupling circuits at low frequency	13
1.9 Coupling circuits at high frequency	18
1.10 Pulses and digital signals	22
1.10.1 Terminology	22
1.10.2 Rise-time, decay-time and time constants	24
1.10.3 Resistance–capacitance coupling network	25
1.10.4 Square wave applied to an $RC$ network	27
1.10.5 Capacitance–resistance circuit	28
1.10.6 Square wave applied to the capacitance–resistance network	29
1.11 Worked example	31
1.12 Summary	32
1.13 Problems	33
<b>2 The p–n junction and the field-effect transistor</b>	<b>36</b>
2.1 Introduction	36
2.2 The p–n junction	36
2.3 Forward and reverse biased p–n junctions	39
2.4 Depletion layer width and junction capacitance	40

## Contents

2.5	The field-effect transistor (unipolar transistor)	page 43
2.6	Principle of operation	43
2.7	Characteristics of the field-effect transistor	47
2.8	The field-effect transistor amplifier	48
2.9	Amplification of signals	51
2.10	Small signal parameters of the f.e.t.	52
2.11	The common-source amplifier (AC analysis)	54
2.12	A simple bias circuit for the f.e.t.	55
2.13	Input and output impedance	56
2.14	Coupling of f.e.t. amplifiers and amplification of low frequency signals	57
2.15	Amplification of high frequency signals	59
†2.16	The source follower	60
2.17	The metal oxide semiconductor transistor (MOST)	62
2.17.1	Complementary MOS (CMOS) transistors	66
2.18	Worked example	68
2.19	Summary	70
2.20	Problems	70
<b>Quiz 1 (chapters 1 and 2)</b>		<b>74</b>
<b>3</b>	<b>The bipolar transistor</b>	<b>76</b>
3.1	Introduction	76
3.2	Principle of operation	76
3.3	Current relationships	79
3.4	Typical common-emitter characteristics	80
3.5	Data for a typical npn transistor	83
3.6	Ratings and selection of operating point	83
†3.7	Operating point stability	85
3.8	Graphical estimates of circuit gain	88
3.9	Small-signal equivalent circuits for the bipolar transistor	91
†3.9.1	T-network	92
3.9.2	Hybrid-parameter network	93
†3.9.3	Hybrid- $\pi$ network	95
3.10	Calculation of amplifier performance	96
3.11	Frequency response	99
†3.12	Emitter follower performance	100
†3.13	Coupling between amplifier stages	104
3.14	Manufacture of planar transistors	106

† Sections so marked may be omitted on first reading.

3.15 Worked example	<i>page</i> 106
3.16 Relative merits of bipolar and field-effect transistors	110
3.17 Summary	110
3.18 Problems	111
<b>4 Operational amplifiers and linear integrated circuits</b>	<b>114</b>
4.1 Introduction	114
4.2 A review of the properties of real and ideal amplifiers	114
4.3 The terminology of integrated circuit differential amplifiers	115
4.4 The inverting operational amplifier	117
4.4.1 Gain	117
4.4.2 Input and output impedances of the inverting amplifier	121
4.5 The non-inverting operational amplifier	123
4.5.1 Gain and output impedance	123
4.5.2 Input impedance	125
4.6 The differential operational amplifier	126
4.7 Some applications of operational amplifiers	128
4.7.1 The voltage follower	128
4.7.2 The adder amplifier	129
4.7.3 Integrating and differentiating amplifiers	131
4.7.4 Simulation of an inductance	132
4.7.5 A band-pass filter	134
4.7.6 Current-to-voltage converter	136
4.8 Frequency response of operational amplifiers	137
4.9 The differential amplifier	140
4.9.1 Gain from a symmetrical differential amplifier	142
4.9.2 The common-mode rejection ratio (CMRR) of the differential amplifier	143
4.9.3 Bipolar transistor differential amplifier	145
4.10 Some practical considerations	146
4.10.1 Input bias currents and input offset current	146
4.10.2 Offset voltage	148
4.10.3 Common-mode rejection ratio	149
4.10.4 Slewing rate and full power response	150
4.11 Linear integrated circuits	152
4.12 Worked examples	154
4.13 Summary	158
4.14 Problems	158
<b>Quiz 2 (chapters 3 and 4)</b>	<b>162</b>

<b>5 Negative feedback</b>	<i>page</i> 164
5.1 Introduction	164
5.2 Definitions of feedback	164
5.3 Realisation of <i>A</i> and <i>B</i>	166
5.3.1 Voltage feedback applied to a voltage amplifier	167
5.3.2 Voltage feedback applied to a differential amplifier	168
5.3.3 Current feedback applied to a current amplifier	169
5.4 Stabilisation of gain	171
5.5 Increase in frequency response	172
5.6 Reduction of the effect of internal disturbances in the amplifier	173
5.7 Effect on the input and output impedances of the amplifier	174
5.7.1 Voltage amplifier with voltage feedback	175
5.7.2 Current amplifier with current feedback	176
†5.7.3 Trans-conductance or trans-resistance amplifiers	177
†5.8 Factors for and against feedback over several stages	180
5.9 Instability	181
†5.10 Interpretation of the Nyquist diagram	183
5.11 Worked example	185
5.12 Summary	186
5.13 Problems	187
<b>6 Positive feedback and oscillators</b>	190
6.1 Introduction	190
6.2 Theoretical requirements for oscillation	190
6.3 Sinusoidal oscillators	192
6.4 Realisation of phase-shifting networks	193
6.4.1 Ladder networks	194
6.4.2 Wien networks	195
†6.4.3 Tuned networks	196
†6.5 Frequency stability	199
6.6 Stabilisation of oscillator output amplitude	200
6.6.1 Voltage sensitive amplifier using a thermistor	203
†6.6.2 Voltage sensitive amplifier using a bulb or a field-effect transistor	204
†6.7 Oscillator using operational amplifiers as integrators	206
6.8 Worked example	207
6.9 Summary	209
6.10 Problems	209

## Quiz 3 (chapters 5 and 6)

page 212

<b>7</b>	<b>Digital fundamentals</b>	214
7.1	Introduction	214
7.2	Transistor as a switch – the simple inverter	214
7.3	Simple gates – NAND, AND, NOR, OR, Exclusive-OR and NOR	216
7.4	Number systems – binary, hexadecimal and BCD	218
7.5.	Definitions of combinational and sequential logic	220
7.6	Combinational logic identities – Boolean algebra	220
7.7	Karnaugh maps for logic simplification	224
†7.8	Hazards and their elimination (using the Karnaugh map)	227
7.9	Memory – two inverting gates with feedback	228
†7.10	Realisation of gates with MOS or bipolar devices – 3-state or open collector devices	229
7.11	Comparison of logic families	232
7.12	Worked examples	234
7.12.1	Analysis of address decoder	234
7.12.2	Synthesis of month-length detector	234
7.12	Summary	235
7.14	Problems	236
<b>8</b>	<b>Digital circuits and applications</b>	239
8.1	Introduction	239
8.2	Bistable circuit ( <i>S-R</i> type, latch, <i>J-K</i> , <i>M-S</i> and clocked types)	239
8.3	Counters – ripple and synchronous types	243
8.4	Registers, accumulators and arithmetic ICs	245
†8.5	State diagrams and sequential design	246
†8.6	Voltage level detector, Schmitt trigger IC	251
8.7	Digital to analogue converters (DACs)	254
8.8	Analogue to digital converters (ADCs)	257
8.9	Memories; RAM, ROM, EPROM	259
8.10	Applications	261
†8.10.1	Use of LSI circuits as combinational logic elements	261
†8.10.2	Multiplexers and transmission gates	263
8.10.3	Random and pseudo-random sequences	264
8.11	Capabilities of microprocessors	265
8.12	Summary	268
8.13	Problems	268
<b>Appendix A</b>	A list of useful textbooks	271
<b>Appendix B</b>	Device data and characteristics	272
<b>Answers to problems</b>		280
<b>Index</b>		284