

2784-1080

Continuous- Time Active Filter Design

**T. Deliyannis
Yichuang Sun
J.K. Fidler**



CRC Press

Boca Raton London New York Washington, D.C.

Contents

Chapter 1 Filter Fundamentals

1.1	Introduction.....	1
1.2	Filter Characterization	1
1.2.1	Lumped.....	1
1.2.2	Linear	2
1.2.3	Continuous-Time and Discrete-Time.....	3
1.2.4	Time-Invariant	3
1.2.5	Finite.....	3
1.2.6	Passive and Active.....	3
1.3	Types of Filters	4
1.4	Steps in Filter Design	6
1.5	Analysis	7
1.5.1	Nodal Analysis.....	7
1.5.2	Network Parameters	10
1.5.2.1	One-Port Network.....	10
1.5.2.2	Two-Port Network.....	11
1.5.3	Two-Port Interconnections	14
1.5.3.1	Series-Series Connection.....	14
1.5.3.2	Parallel-Parallel Connection.....	15
1.5.3.3	Series Input-Parallel Output Connection	16
1.5.3.4	Parallel Input-Series Output Connection	16
1.5.3.5	Cascade Connection.....	16
1.5.4	Network Transfer Functions	17
1.6	Continuous-Time Filter Functions	19
1.6.1	Pole-Zero Locations.....	20
1.6.2	Frequency Response.....	21
1.6.3	Transient Response.....	22
1.6.3.1	Impulse Response.....	22
1.6.3.2	Step Response	23
1.6.4	Step and Frequency Response	24
1.7	Stability	26
1.7.1	Short-Circuit and Open-Circuit Stability	27
1.7.2	Absolute Stability and Potential Instability	27
1.8	Passivity Criteria for One- and Two-Port Networks.....	29
1.8.1	One-Ports.....	29
1.8.2	Two-Ports.....	30
1.8.3	Activity.....	31
1.8.4	Passivity and Stability.....	31
1.9	Reciprocity.....	32
1.10	Summary	33
	References and Further Reading.....	33

Chapter 2 The Approximation Problem

2.1	Introduction.....	35
-----	-------------------	----

2.2	Filter Specifications and Permitted Functions.....	35
2.2.1	Causality	35
2.2.2	Rational Functions.....	36
2.2.3	Stability	36
2.3	Formulation of the Approximation Problem.....	37
2.4	Approximation of the Ideal Lowpass Filter.....	38
2.4.1	Butterworth or Maximally Flat Approximation	39
2.4.2	Chebyshev or Equiripple Approximation	42
2.4.3	Inverse Chebyshev Approximation	45
2.4.4	Papoulis Approximation	47
2.4.5	Elliptic Function or Causer Approximation	47
2.4.6	Selecting the Filter from Its Specifications	49
2.4.7	Amplitude Equalization	52
2.5	Filters with Linear Phase: Delays.....	52
2.5.1	Bessel-Thomson Delay Approximation	54
2.5.2	Other Delay Functions.....	58
2.5.3	Delay Equalization	59
2.6	Frequency Transformations	59
2.6.1	Lowpass-to-Lowpass Transformation.....	60
2.6.2	Lowpass-to-Highpass Transformation.....	61
2.6.3	Lowpass-to-Bandpass Transformation.....	62
2.6.4	Lowpass-to-Bandstop Transformation.....	63
2.6.5	Delay Denormalization.....	64
2.7	Design Tables for Passive LC Ladder Filters	64
2.7.1	Transformation of Elements.....	65
2.7.1.1	LC Filters.....	65
2.7.1.2	Active RC Filters.....	68
2.8	Impedance Scaling	70
2.9	Predistortion.....	71
2.10	Summary	72
	References.....	73

Chapter 3 Active Elements

3.1	Introduction.....	75
3.2	Ideal Controlled Sources	75
3.3	Impedance Transformation (Generalized Impedance Converters and Inverters).....	76
3.3.1	Generalized Impedance Converters	78
3.3.1.1	The Ideal Active Transformer	78
3.3.1.2	The Ideal Negative Impedance Converter.....	79
3.3.1.3	The Positive Impedance Converter.....	79
3.3.1.4	The Frequency-Dependent Negative Resistor	80
3.3.2	Generalized Impedance Inverters.....	81
3.3.2.1	The Gyrator	81
3.3.2.2	Negative Impedance Inverter.....	82
3.4	Negative Resistance	82
3.5	Ideal Operational Amplifier.....	84
3.5.1	Operations Using the Ideal Opamp.....	85
3.5.1.1	Summation of Voltages.....	85
3.5.1.2	Integration	86
3.5.2	Realization of Some Active Elements Using Opamps	87

3.5.2.1	Realization of Controlled Sources.....	87
3.5.2.2	Realization of Negative-Impedance Converters.....	88
3.5.2.3	Gyrator Realizations	90
3.5.2.4	GIC Circuit Using Opamps.....	91
3.5.3	Characteristics of IC Opamps.....	93
3.5.3.1	Open-Loop Voltage Gain of Practical Opamps.....	93
3.5.3.2	Input and Output Impedances.....	94
3.5.3.3	Input Offset Voltage V_{IO}	95
3.5.3.4	Input Offset Current I_{IO}	95
3.5.3.5	Input Voltage Range V_I	96
3.5.3.6	Power Supply Sensitivity $\Delta V_{IO} / \Delta V_{CG}$	97
3.5.3.7	Slew Rate SR	97
3.5.3.8	Short-Circuit Output Current.....	97
3.5.3.9	Maximum Peak-to-Peak Output Voltage Swing V_{opp}	97
3.5.3.10	Input Capacitance C_i	98
3.5.3.11	Common-Mode Rejection Ratio $CMRR$	98
3.5.3.12	Total Power Dissipation	98
3.5.3.13	Rise Time t_r	98
3.5.3.14	Overshoot.....	98
3.5.4	Effect of the Single-Pole Compensation on the Finite Voltage Gain Controlled Sources	98
3.6	The Ideal Operational Transconductance Amplifier (OTA).....	100
3.6.1	Voltage Amplification	100
3.6.2	A Voltage-Variable Resistor (VVR).....	101
3.6.3	Voltage Summation	101
3.6.4	Integration	102
3.6.5	Gyrator Realization	102
3.6.6	Practical OTAs.....	103
3.6.7	Current Conveyor	104
3.7	Summary	106
	References.....	106

Chapter 4 Realization of First- and Second-Order Functions Using Opamps

4.1	Introduction.....	107
4.2	Realization of First-Order Functions	107
4.2.1	Lowpass Circuits	108
4.2.2	Highpass Circuits.....	109
4.2.3	Allpass Circuits.....	110
4.3	The General Second-Order Filter Function.....	110
4.4	Sensitivity of Second-Order Filters	111
4.5	Realization of Biquadratic Functions Using SABs.....	114
4.5.1	Classification of SABs	115
4.5.2	A Lowpass SAB.....	116
4.5.3	A Highpass SAB	120
4.5.4	A Bandpass SAB	121
4.5.5	Lowpass- and Highpass-Notch Biquads.....	126
4.5.6	Lowpass Notch ($R_6 = \infty$)	127
4.5.7	Highpass Notch ($R_7 = \infty$)	129
4.5.8	An Allpass SAB.....	129
4.6	Realization of a Quadratic with a Positive Real Zero	132
4.7	Biquads Obtained Using the Twin-T RC Network.....	134

4.8	Two-Opamp Biquads	136
4.8.1	Biquads by Inductance Simulation	136
4.8.2	Two-Opamp Allpass Biquads	138
4.8.3	Selectivity Enhancement	139
4.9	Three-Opamp Biquads.....	141
4.9.1	The Tow-Thomas [25–27] Three-Opamp Biquad.....	144
4.9.2	Excess Phase and Its Compensation in Three-Opamp Biquads	145
4.9.3	The Åkerberg-Mossberg Three-Opamp Biquad	146
4.10	Summary	147
	References.....	148

Chapter 5 Realization of High-Order Functions

5.1	Introduction.....	151
5.2	Selection Criteria for High-Order Function Realizations	151
5.3	Multiparameter Sensitivity	153
5.4	High-Order Function Realization Methods.....	154
5.5	Cascade Connection of Second-Order Sections	155
5.5.1	Pole-Zero Pairing.....	156
5.5.2	Cascade Sequence.....	158
5.5.3	Gain Distribution.....	159
5.6	Multiple-Loop Feedback Filters	162
5.6.1	The Shifted-Companion-Form (SCF) Design Method	166
5.6.2	Follow-the-Leader Feedback Design (FLF)	168
5.7	Cascade of Biquartics.....	171
5.7.1	The BR Section	171
5.7.2	Effect of η on ω'_i and Q'_i	173
5.7.3	Cascading Biquartic Sections.....	175
5.7.4	Realization of Biquartic Sections.....	175
5.7.4.1	Design Example.....	176
5.7.5	Sensitivity of CBR Filters.....	178
5.8	Summary	180
	References.....	180
	Further Reading	181

Chapter 6 Simulation of LC Ladder Filters Using Opamps

6.1	Introduction.....	183
6.2	Resistively-Terminated Lossless LC Ladder Filters	184
6.3	Methods of LC Ladder Simulation	184
6.4	The Gyrator	185
6.4.1	Gyrator Imperfections	186
6.4.2	Use of Gyration in Filter Synthesis	188
6.5	Generalized Impedance Converter, GIC.....	190
6.5.1	Use of GICs in Filter Synthesis	190
6.6	FDNRs: Complex Impedance Scaling	193
6.7	Functional Simulation.....	195
6.7.1	Example	198
6.7.2	Bandpass Filters.....	199
6.7.3	Dynamic Range of LF Filters	201
6.8	Summary	202
	References.....	202

Chapter 7 Wave Active Filters

7.1	Introduction.....	205
7.2	Wave Active Filters.....	205
7.3	Wave Active Equivalents (WAEs)	208
7.3.1	Wave Active Equivalent of a Series-Arm Impedance	208
7.3.2	Wave Active Equivalent of a Shunt-Arm Admittance	209
7.3.3	WAEs for Equal Port Normalization Resistances	209
7.3.4	Wave Active Equivalent of the Signal Source.....	210
7.3.5	Wave Active Equivalent of the Terminating Resistance	211
7.3.6	WAEs of Shunt-Arm Admittances.....	212
7.3.7	Interconnection Rules	212
7.3.8	WAEs of Tuned Circuits	214
7.3.9	WA Simulation Example	216
7.3.10	Comments on the Wave Active Filter Approach	216
7.4	Economical Wave Active Filters	217
7.5	Sensitivity of WAFs	220
7.6	Operation of WAFs at Higher Frequencies.....	221
7.7	Complementary Transfer Functions	223
7.8	Wave Simulation of Inductance.....	224
7.9	Linear Transformation Active Filters (LTA Filters).....	224
7.9.1	Interconnection Rule	227
7.9.2	General Remarks on the Method	229
7.10	Summary	229
	References.....	229

Chapter 8 Single Operational Transconductance Amplifier (OTA) Filters

8.1	Introduction.....	231
8.2	Single OTA Filters Derived from Three-Admittance Model.....	232
8.2.1	First-Order Filter Structures.....	232
8.2.1.1	First-Order Filters with One or Two Passive Components	233
8.2.1.2	First-Order Filters with Three Passive Components.....	234
8.2.2	Lowpass Second-Order Filter with Three Passive Components	235
8.2.3	Lowpass Second-Order Filters with Four Passive Components	236
8.2.4	Bandpass Second-Order Filters with Four Passive Components.....	238
8.3	Second-Order Filters Derived from Four-Admittance Model	241
8.3.1	Filter Structures and Design	241
8.3.1.1	Lowpass Filter	241
8.3.1.2	Bandpass Filter	243
8.3.1.3	Other Considerations on Structure Generation	244
8.3.2	Second-Order Filters with the OTA Transposed.....	245
8.3.2.1	Highpass Filter.....	245
8.3.2.2	Lowpass Filter	247
8.3.2.3	Bandpass Filter	247
8.4	Tunability of Active Filters Using Single OTA	249
8.5	OTA Nonideality Effects.....	249
8.5.1	Direct Analysis Using Practical OTA Macro-Model.....	249
8.5.2	Simple Formula Method.....	253
8.5.3	Reduction and Elimination of Parasitic Effects.....	253
8.6	OTA-C Filters Derived from Single OTA Filters	254
8.6.1	Simulated OTA Resistors and OTA-C Filters	254

8.6.2	Design Considerations of OY Structures	255
8.7	Second-Ordre Filters Derived from Five-Admittance Model	258
8.7.1	Highpass Filter.....	259
8.7.2	Bandpass Filter.....	260
8.7.3	Lowpass Filter.....	262
8.7.4	Comments and Comparison.....	263
8.8	Summary	264
	References.....	264

Chapter 9 Two Integer Loop OTA-C Filters

9.1	Introduction.....	269
9.2	OTA-C Building Blocks and First-Order OTA-C Filters	270
9.3	Two Integrator Loop Configurations and Performance	272
9.3.1	Configurations	272
9.3.2	Pole Equations	272
9.3.3	Design	273
9.3.4	Sensitivity	273
9.3.5	Tuning	273
9.3.6	Biquadratic Specifications	273
9.4	OTA-C Realizations of Distributed-Feedback (DF) Configuration	274
9.4.1	DF OTA-C Circuit and Equations	274
9.4.2	Filter Functions.....	276
9.4.3	Design Examples	277
9.4.4	DF OTA-C Realizations with Special Feedback Coefficients	278
9.5	OTA-C Filters Based on Summed-Feedback (SF) Configuration	280
9.5.1	SF OTA-C Realization with Arbitrary k_{12} and k_{11}	281
9.5.1.1	Design Example of KHN OTA-C Biquad.....	282
9.5.2	SF OTA-C Realization with $k_{12} = k_{11} = k$	282
9.6	Biquadratic OTA-C Filters Using Lossy Integrators.....	283
9.6.1	Tow-Thomas OTA-C Structure.....	284
9.6.2	Feedback Lossy Integrator Biquad	284
9.7	Comparison of Basic OY Filter Structures	285
9.7.1	Multifunctionality and Number of OTA.....	285
9.7.2	Sensitivity	286
9.7.3	Tunability.....	286
9.8	Versatile Filter Functions Based on Node Current Injection.....	287
9.8.1	DF Structures with Node Current Injection	288
9.8.2	SF Structures with Node Current Injection	289
9.9	Universal Biquads Using Output Summation Approach.....	291
9.9.1	DF-Type Universal Biquads.....	292
9.9.2	SF Type Universal Biquads	292
9.9.3	Universal Biquads Based on Node Current Injection and Output Summation	293
9.9.4	Comments on Universal Biquads	294
9.10	Universal Biquads Based on Canonical and TT Circuits	294
9.11	Effects and Compensation of OTA Nonidealities	
9.11.1	General Model and Equations.....	295
9.11.2	Finite Impedance Effects and Compensation.....	298
9.11.3	Finite Bandwidth Effects and Compensation.....	299
9.11.4	Selection of OTA-C Filter Structures.....	301
9.11.5	Selection of Input and Output Methods	302

9.11.6 Dynamic Range Problem.....	302
9.12 Summary	303
References.....	304

Chapter 10 OTA-C Filters Based on Ladder Simulation

10.1 Introduction.....	309
10.2 Component Substitution Method	310
10.2.1 Direct Inductor Substitution	310
10.2.1.1 OTA-C Inductors	310
10.2.1.2 Tolerance Sensitivity of Filter Function.....	311
10.2.1.3 Parasitic Effects on Simulated Inductor	312
10.2.1.4 Parasitic Effects on Filter Function	313
10.2.2 Application Examples of Inductor Substitution	315
10.2.2.1 OTA-C Biquad Derived from RLC Resonator Circuit.....	315
10.2.2.2 A Lowpass OTA-C Filter	316
10.2.3 Bruton Transformation and FDNR Simulation.....	317
10.3 Admittance/Impedance Simulation.....	320
10.3.1 General Description of the Method	320
10.3.2 Application Examples and Comparison.....	321
10.3.3 Parial Floating Admittance Concept	324
10.4 Signal Flow Simulation and Leapfrog Structures.....	325
10.4.1 Leapfrog Simulation Structures of General Ladder	325
10.4.2 OTA-C Lowpass LF Filters.....	328
10.4.2.1 Example	330
10.4.3 OTA-C Bandpass LF Filter Design.....	332
10.4.4 Partial Floating Admittance Block Diagram and OTA-C Realization	332
10.4.5 Alternative Leapfrog Structures and OTA-C Realizations	334
10.5 Equivalence of Admittance and Signal Simulation Methods	336
10.6 OTA-C Simulation of LC Ladders Using Matrix Methods.....	338
10.7 Coupled Biquad OTA Structures.....	340
10.8 Some General Practical Design Considerations.....	342
10.8.1 Selection of Capacitors and OTAs.....	342
10.8.2 Tolerance Sensitivity and Parasitic Effects.....	343
10.8.3 OTA Finite Impedances and Frequency-Dependent Transconductance	343
10.9 Summary	343
References.....	344

Chapter 11 Multiple Integrator Loop Feedback OTA-C Filters

11.1 Introduction.....	349
11.2 General Design Theory of All-Pole Structures	350
11.2.1 Multiple Loop Feedback OTA-C Model.....	350
11.2.2 System Equations and Transfer Function	350
11.2.3 Feedback Coefficient Matrix and Systematic Structure Generation	353
11.2.4 Filter Synthesis Prcedure Based on Coefficient Matching	354
11.3 Structure Generation and Design of All-Pole Filters.....	355
11.3.1 First- and Second-Order Filters	355
11.3.2 Third-Order Filters	356
11.3.3 Fourth-Order Filters.....	357
11.3.4 Design Examples of Fourth-Order Filters.....	359
11.3.5 General n th-Order Architectures.....	360

11.3.5.1	General IFLF Configuration.....	360
11.3.5.2	General LF Configuration	361
11.3.6	Other Types of Realization.....	362
11.4	Generation and Synthesis of Transmission Zeros.....	363
11.4.1	Output Summation of OTA Network.....	364
11.4.2	Input Distribution of OTA Network.....	364
11.4.3	Universal and Special Third-Order OTA-C Filters	366
11.4.3.1	IFLF and Output Summation Structure in Fig. 11.10(a)	367
11.4.3.2	IFLF and Input Distribution Structure in Fig. 11.10(b)	367
11.4.3.3	LF and Output Summation Structure in Fig. 11.10(c)	367
11.4.3.4	LF and Input Distribution Structure in Fig. 11.10(d).....	368
11.4.3.5	Realization of Special Characteristics	368
11.4.3.6	Design of Elliptic Filters	368
11.4.4	General n th-Order OTA-C Filters.....	370
11.4.4.1	Universal IFLF Architectures	370
11.4.4.2	Universal LF Architectures	372
11.5	General Formulation of Sensitivity Analysis	373
11.5.1	General Sensitivity Relations.....	373
11.5.2	Sensitivities of Different Filter Structures	375
11.6	Determination of Maximum Signal Magnitude.....	377
11.7	Effects of OTA Frequency Response Nonidealities	379
11.8	Summary	381
	References.....	382

Chapter 12 Current-Mode Filters and Other Architectures

12.1	Introduction.....	387
12.2	Current-Mode Filters Based on Single DO-OTA Model.....	388
12.2.1	General Model and Filter Architecture Generation.....	388
12.2.1.1	First-Order Filter Structures.....	389
12.2.1.2	Second-Order Filter Architectures	390
12.2.2	Passive Resistor and Active Resistor	390
12.2.3	Design of Second-Order Filters	391
12.2.4	Effects of DO-OTA Nonidealities	394
12.3	Current-Mode Two Integrator Loop DO-OTA-C Filters.....	396
12.3.1	Basic Building Blocks and First-Order Filters	396
12.3.2	Current-Mode DO-OTA-C Configurations with Arbitrary k_{ij}	397
12.3.3	Current-Mode DO-OTA-C Biquadratic Architectures with $k_{12} = k_{ij}$	398
12.3.4	Current-Mode DO-OTA-C Biquadratic Architectures with $k_{12} = 1$	399
12.3.5	DO-OTA Nonideality Effects	401
12.3.6	Universal Current-Mode DO-OTA-C Filters.....	401
12.4	Current-Mode DO-OTA-C Ladder Simulation Filters	405
12.4.1	Leapfrog Simulation Structures of General Ladder	405
12.4.2	Current-Mode DO-OTA-C Lowpass LF Filters.....	407
12.4.3	Current-Mode DO-OTA-C Bandpass LF Filter Design.....	409
12.4.4	Alternative Current-Mode Leapfrog DO-OTA-C Structure.....	410
12.5	Current-Mode Multiple Loop Feedback DO-OTA-C Filters.....	411
12.5.1	Design of All-Pole Filters.....	411
12.5.2	Realization of Transmission Zeros	415
12.5.2.1	Multiple Loop Feedback with Input Distribution	415
12.5.2.2	Multiple Loop Feedback with Output Summation	416
12.5.2.3	Filter Structures and Design Formulas.....	417

12.6 Other Continuous-Time Filter Structures419
12.6.1 Balanced Opamp-RC and OTA-C Structures419
12.6.2 MOSFET-C Filters.....420
12.6.3 OTA-C Opamp Filter Design422
12.6.4 Active Filters Using Current Conveyors.....423
12.6.5 Log-Domain, Current Amplifier, and Integrated-RLC Filters425
12.7 Summary425
References.....426

Appendix A A Sample of Filter Functions.....431
Index.....437