
Transmission Lines in Computer Engineering

Sol Rosenstark

*Department of Electrical and Computer Engineering
New Jersey Institute of Technology
Newark, New Jersey*

McGraw-Hill, Inc.

New York San Francisco Washington, D.C. Auckland Bogotá
Caracas Lisbon London Madrid Mexico City Milan
Montreal New Delhi San Juan Singapore
Sydney Tokyo Toronto

Contents

Preface	xi
Chapter 1. Transmission Line Fundamentals	1
1.1 Introduction	1
1.2 Transmission Line Concepts	2
1.3 Traveling Waves on Lossless Lines	5
1.4 The Characteristic-Impedance Concept	9
1.5 Sinusoidal Waves—Power Propagation	12
1.6 Distortionless Transmission	15
1.7 Distortionless Lossy Lines	16
1.8 Conclusion	18
Bibliography	18
Problems	18
Chapter 2. Reflections on Transmission Lines	21
2.1 Wave Reflections on Terminated Lossless Lines	21
2.2 Reflection or Lattice Diagrams	25
2.3 Effect of Source Resistance	28
2.4 The Steady State on Lossless Lines	29
2.5 Non-constant Source Excitations—Precursors	31
2.6 Series and Parallel Terminated Lines	35
2.7 Cascaded Lines—Transmission Coefficients	36
2.8 Sources Driving Multiple Lines	42
2.9 One Line Driving Multiple Lines	45
2.10 Conclusion	49
Bibliography	49
Problems	49

Chapter 3. Transients on Transmission Lines	53
3.1 Introduction	53
3.2 Capacitive Load—Series Match	54
3.3 Capacitive Load—Parallel Match	62
3.4 Distributed Capacitive Load—Series Match	67
3.5 Distributed Capacitive Load—Parallel Match	72
3.6 Uniform Capacitive Loading—In the Limit	77
3.7 Conclusion	84
Problems	85
Chapter 4. Non-linear Sources and Loads	89
4.1 Introduction	89
4.2 The Method of Load-Line Analysis	89
4.3 Transmission-Line Load-Line Analysis	93
4.4 Series and Parallel Terminated Lines	98
4.5 TTL and CMOS Analysis Using Bergeron Plots	103
4.6 Conclusion	107
References	110
Problems	110
Chapter 5. Crosstalk on Transmission Lines	113
5.1 Introduction	113
5.2 Derivation of the Basic Crosstalk Relations	114
5.3 The Forward Crosstalk Equation	119
5.4 The Reverse Crosstalk Equation	121
5.5 Unmatched Aggressor Lines	124
5.6 Unmatched Victim Lines	126
5.7 Measurement of Crosstalk Coefficients	126
5.8 Conclusion	129
Bibliography	130
Problems	130
Chapter 6. Interconnecting High Speed ECL	133
6.1 Introduction	133
6.2 Modeling of ECL Circuits	133
6.3 Model for Line with Initial Conditions	134
6.4 Termination Requirements of Logic Circuit PC Boards	136
6.5 Parallel Termination	137
6.6 Parallel-Terminated Multiple-Gates	143
6.7 Series Termination	144
6.8 Parallel Fanout with Series-Terminated Lines	151
6.9 Discussion of Parallel and Series Terminations	155
6.10 Unterminated Lines	156
6.11 Conclusion	160
References	160

Program Listing	161
Problems	162
Chapter 7. Transmission Line Characteristics	167
7.1 Introduction	167
7.2 Coaxial Transmission-Line	169
7.3 Parallel Wire and Twisted Pair	170
7.4 Wire over Ground Plane	171
7.5 Stripline	172
7.6 Microstrip	174
7.7 The Parallel-Plate Transmission-Line	176
7.8 Conclusion	177
References	177
Problems	178
Appendix A. Introduction to High Speed ECL	181
A.1 Introduction	181
A.2 Requirement for Pulldown Resistors	185
Bibliography	186
Problems	187
Appendix B. Laplace Transform Review	189
B.1 The Laplace Transform	189
B.2 Inversion of Laplace Transforms	197
B.3 Application of Laplace Transforms to Circuits	202
B.4 Conclusion	204
References	204
Problems	204
Index	209