

# Introduction to Digital Techniques

**Dan I. Porat, Ph.D.**

Stanford Linear Accelerator Center  
Stanford University, California

**Arpad Barna, Ph.D.**

Hewlett-Packard Laboratories  
Palo Alto, California

**John Wiley and Sons**

New York   Chichester   Brisbane   Toronto

# Contents

<b>Chapter 1</b>		
<b>Perspective</b>	1-1 Introduction	1
	1-2 Integrated Circuits	3
<b>Chapter 2</b>		
<b>Logic Circuits</b>	2-1 Logic Circuits Using Switches	7
	2-2 Logic Circuits Using Rays	10
	2-3 Logic Circuits Using Diodes	14
	2-4 Diode-Transistor Logic (DTL)	18
	2-5 Transistor-Transistor Logic (TTL)	25
	2-6 Emitter-Coupled Logic (ECL)	32
	*2-7 Integrated Injection Logic (I <sup>2</sup> L)	38
	2-8 MOS Logic	40
	2-9 Complementary MOS (CMOS) Logic	43
	Summary	55
	Problems	55
<b>Chapter 3</b>		
<b>Number Systems</b>	3-1 Decimal Numbers	60
	3-2 Binary Numbers	61
	3-3 The Octal and Hexadecimal Number Systems	65
	3-4 Conversion between Number Bases	67
	3-5 Negative Numbers	74
	Summary	80
	Problems	81
<b>Chapter 4</b>		
<b>Coding</b>	4-1 The Need for Coding	83
	4-2 Binary-Coded Decimal (BCD) Numbers	83
	4-3 Unit-Distance Codes	89
	4-4 Error-Detecting Codes	94
	4-5 Alphanumeric Codes	97
	Summary	101
	Problems	101

\* An asterisk before a section title refers to optional material.

<b>Chapter 5</b>		
<b>Boolean Algebra and Simplification Methods</b>		
5-1	Boolean Algebra	105
5-2	Truth Tables	106
5-3	Logic Operators	108
5-4	Postulates of Boolean Algebra	110
5-5	Theorems of Boolean Algebra	111
5-6	Analysis and Synthesis of Combinational Logic Circuits	121
5-7	Standard Forms	123
5-8	Karnaugh Maps	125
	Summary	136
	Problems	137
<b>Chapter 6</b>		
<b>Combinational Logic Circuits</b>		
6-1	Additional Logic Operators	141
6-2	Positive and Negative Logic	149
6-3	2-Stage NAND Logic Circuits	151
6-4	2-Stage NOR Logic Circuits	153
6-5	AND-OR-INVERT (AOI) Gates	155
6-6	Digital Multiplexers	157
6-7	Decoders	162
6-8	Priority Encoders	166
	Summary	167
	Problems	168
<b>Chapter 7</b>		
<b>Flip-Flops (FFs)</b>		
7-1	Introduction	172
7-2	R-S storage FFs	172
7-3	Clocked R-S FFs	180
7-4	State Tables and Function Tables of Clocked FFs	182
7-5	Clocked D FFs	183
7-6	Use of Clocked FFs for Storage	184
7-7	Master-slave R-S and D FFs	185
7-8	Master-slave FFs with Data Lockout	188
7-9	Edge-triggered FFs	193
7-10	J-K FFs	194
7-11	T FFs	195
7-12	Direct Preset and Clear Inputs	195
7-13	Timing	197
	Summary	204
	Problems	205
<b>Chapter 8</b>		
<b>Counters</b>		
8-1	Introduction	206
8-2	Divide-by-2 Counters	207
8-3	Ripple Counters	209
8-4	One-Bit Counters	222

	8-5 State Diagrams	223
	8-6 Synchronous Counters	226
	8-7 Hybrid Counters	262
	Summary	264
	Problems	264
<b>Chapter 9</b>		
<b>Shift Registers and</b>	9-1 Introduction	268
<b>Shift Register Counters</b>	9-2 Shift Registers	268
	9-3 Shift Register Counters	275
	9-4 Operating Speed	285
	Summary	285
	Problems	286
<b>Chapter 10</b>		
<b>Large-Scale</b>	10-1 Introduction	290
<b>Integrated Circuits (LSI)</b>	10-2 Dynamic MOS Inverters and Gates	291
	10-3 MOS Shift Registers	293
	10-4 Random-Access Memories (RAMs)	300
	10-5 Read-Only Memories (ROMs)	311
	10-6 Programmable Logic Arrays (PLAs)	317
	*10-7 Content-Addressable Memories (CAMs)	321
	*10-8 First-In First-Out Memories (FIFOs)	323
	10-9 Charge-Coupled Devices (CCDs)	325
	10-10 Magnetic Bubble Memories (MBMs)	328
	Summary	333
	Problems	333
<b>Chapter 11</b>		
<b>Arithmetic Circuits</b>	11-1 Introduction	336
	11-2 Digital Comparators	337
	11-3 Adders	342
	11-4 Subtractors	347
	11-5 Arithmetic Logic Units (ALUs)	348
	11-6 Multipliers	348
	Summary	350
	Problems	
<b>Chapter 12</b>		
<b>Code Converters and</b>	12-1 Introduction	353
<b>Display Devices</b>	12-2 Excess-3 Gray-Code to 8-4-2-1 BCD Converter	354
	12-3 Binary to Gray-Code Converter	356
	12-4 Gray-Code to Binary Converter	357
	12-5 Binary to BCD Converters	359
	12-6 BCD to Binary Converters	364
	12-7 Display Decoders and Drivers	370
	Summary	376
	Problems	376

\* An asterisk before a section title refers to optional material.

<b>Chapter 13</b>		
<b>Computers and Microcomputers</b>	13-1	Introduction 380
	13-2	Basic Characteristics 380
	13-3	Basic Structure 382
	13-4	Basic Programming Techniques 385
	13-5	Input and Output (I/O) 392
	13-6	The Main Memory 400
	13-7	The Control Unit 404
		Summary 409
		Problems 409
<b>Chapter 14</b>		
<b>Digital-to-Analog and Analog-to Digital Converters</b>	14-1	Introduction 412
	14-2	Digital-to-Analog Converters (DACs) 413
	14-3	Operational Amplifiers 420
	14-4	Current Switches for DACs 425
	14-5	Digital-to-Analog Converters Using Ladder Networks 426
	14-6	DACs Using Quad Current Sources 428
	14-7	Multiplying DAC 431
	14-8	Measuring DAC Parameters 432
	14-9	Analog-to-Digital Converters (ADs) 433
	14-10	Circuit Components for ADCs 435
	14-11	Counter Ramp ADC 444
	14-12	Tracking ADC 445
	14-13	Successive Approximation ADC 446
	14-14	Parallel ADC 450
		Summary 450
		Problems 450
<b>Chapter 15</b>		
<b>System Operation</b>	15-1	Introduction 455
	15-2	Tolerances, Noise Margins, and Loading Rules 455
	15-3	Power Distribution 458
	15-4	Grounding 459
	15-5	Schmitt Trigger Circuits 464
	15-6	Monostable Multivibrators 469
	15-7	Troubleshooting Instrumentation 476
		Summary 482
		Problems 482
<b>Answers to odd-numbered problems</b>		485
<b>Appendix</b>		510
<b>Glossary</b>		511
<b>Index</b>		521