

AC and DC Network Theory

A. J. Pointon

Professor, Microwave Physics,
Portsmouth Polytechnic

and

H. M. Howarth

Principal Lecturer, Physics,
Portsmouth Polytechnic



CHAPMAN & HALL

London · New York · Tokyo · Melbourne · Madras

Contents

Preface	ix
1 Introduction	1
1.1 Electric current	1
1.2 Electrical potential and emf	2
1.3 Resistance and conductance	3
1.4 Internal resistance	4
1.5 Inductance	4
1.6 Capacitance	5
2 Direct current theory	6
2.1 Kirchhoff's laws	6
2.2 Voltage and current generators	8
2.3 Resistors in series and parallel	10
2.4 Non-linear resistive elements	12
2.5 Maximum power theorem	13
3 Capacitors, inductors and transients	14
3.1 Capacitors in series and parallel	14
3.2 Inductors in series and parallel	16
3.3 Circuit transients	17
4 Alternating current theory	23
4.1 Graphical representation of ac voltages	23
4.2 Graphical addition of ac waveforms	25
4.3 Algebraic addition of ac voltages and currents	25
4.4 Phasor representation and the addition of ac voltages and currents	26
4.5 Resistance, self-inductance and capacitance	29

4.6	Complex representation of ac voltages and currents—the j notation	32
4.7	Manipulation of complex impedances	34
4.8	Mutual inductance in an ac circuit	35
4.9	Kirchhoff's laws in ac circuits	36
4.10	Complex impedances in series and parallel	36
4.11	Admittance of an ac circuit	38
4.12	Root mean square values of ac quantities	38
4.13	Power in ac circuits	39
4.14	Complex power and the power triangle	42
4.15	Power usage: improvement of the power factor	43
4.16	Impedance matching	44
4.17	Complex frequency— s notation	46
5	Mesh or loop analysis and nodal analysis	48
5.1	Mesh (loop) analysis	48
5.2	Mesh and loop analysis applied to a generalized circuit	50
5.3	Application of mesh (loop) analysis to circuits containing mutual inductances	52
5.4	Input impedance of a network	54
5.5	Output impedance	55
5.6	Transfer impedance	56
5.7	Nodal analysis	57
5.8	Nodal analysis applied to a generalized circuit	59
5.9	Input, output and transfer admittances	59
6	Network theorems and transformations	63
6.1	Thévenin's theorem	63
6.2	Norton's theorem	66
6.3	Millman's theorem	69
6.4	The reciprocity theorem	72
6.5	The superposition theorem	73
6.6	The substitution theorem	74
6.7	The compensation theorem	74
6.8	The star–delta (λ – Δ) transformation	74
6.9	Transformation involving a mutual inductance	77
7	Electrical resonance	79
7.1	The series L – C – R circuit	79
7.2	Voltage magnification in a series L – C – R circuit	83
7.3	The parallel L – C – R circuit	84

7.4	Current magnification in a parallel $L-C-R$ circuit	86
7.5	Alternative definitions for resonance	86
7.6	Uses of series and parallel resonant circuits	87
7.7	Definitions of Q	88
8	Coupled circuits	90
8.1	The generalized coupled circuit	90
8.2	The low frequency transformer	92
8.3	Resonant circuits coupled by a mutual inductance	97
8.4	Resonant circuits with direct coupling	103
8.5	Uses of coupled resonant circuits	105
9	Two-port networks	106
9.1	Parametric representations of a two-port network	107
9.2	Parameter conversion	110
9.3	The loaded two-port network	111
9.4	Two-port networks connected in cascade	114
9.5	Characteristic impedance	116
9.6	Propagation constant	117
9.7	Symmetrical T and Π networks	118
9.8	Ladder networks	122
9.9	Filters	123
9.10	Attenuators	128
9.11	Transmission lines	129
9.12	Artificial delay lines	134
	Appendix A Quantities and symbols used in the text	136
	Appendix B Exercises	139
	Appendix C Answers to exercises	154
	Index	157