
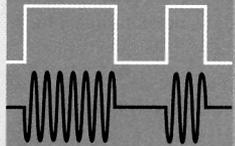


FOURTH EDITION

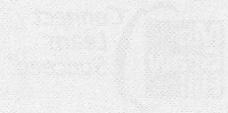

MICROELECTRONIC CIRCUIT DESIGN

RICHARD C. JAEGER
Auburn University

TRAVIS N. BLALOCK
University of Virginia



CONTENTS

Preface xx

PART ONE

SOLID STATE ELECTRONIC AND DEVICES 1

CHAPTER 1

INTRODUCTION TO ELECTRONICS 3

- 1.1 A Brief History of Electronics: From Vacuum Tubes to Giga-Scale Integration 5
- 1.2 Classification of Electronic Signals 8
 - 1.2.1 Digital Signals 9
 - 1.2.2 Analog Signals 9
 - 1.2.3 A/D and D/A Converters—Bridging the Analog and Digital Domains 10
- 1.3 Notational Conventions 12
- 1.4 Problem-Solving Approach 13
- 1.5 Important Concepts from Circuit Theory 15
 - 1.5.1 Voltage and Current Division 15
 - 1.5.2 Thévenin and Norton Circuit Representations 16
- 1.6 Frequency Spectrum of Electronic Signals 21
- 1.7 Amplifiers 22
 - 1.7.1 Ideal Operational Amplifiers 23
 - 1.7.2 Amplifier Frequency Response 25
- 1.8 Element Variations in Circuit Design 26
 - 1.8.1 Mathematical Modeling of Tolerances 26
 - 1.8.2 Worst-Case Analysis 27
 - 1.8.3 Monte Carlo Analysis 29
 - 1.8.4 Temperature Coefficients 32
- 1.9 Numeric Precision 34
 - Summary* 34
 - Key Terms* 35
 - References* 36
 - Additional Reading* 36
 - Problems* 37

CHAPTER 2

SOLID-STATE ELECTRONICS 42

- 2.1 Solid-State Electronic Materials 44
- 2.2 Covalent Bond Model 45
- 2.3 Drift Currents and Mobility in Semiconductors 48
 - 2.3.1 Drift Currents 48
 - 2.3.2 Mobility 49
 - 2.3.3 Velocity Saturation 49
- 2.4 Resistivity of Intrinsic Silicon 50
- 2.5 Impurities in Semiconductors 51
 - 2.5.1 Donor Impurities in Silicon 52
 - 2.5.2 Acceptor Impurities in Silicon 52
- 2.6 Electron and Hole Concentrations in Doped Semiconductors 52
 - 2.6.1 *n*-Type Material ($N_D > N_A$) 53
 - 2.6.2 *p*-Type Material ($N_A > N_D$) 54
- 2.7 Mobility and Resistivity in Doped Semiconductors 55
- 2.8 Diffusion Currents 59
- 2.9 Total Current 60
- 2.10 Energy Band Model 61
 - 2.10.1 Electron–Hole Pair Generation in an Intrinsic Semiconductor 61
 - 2.10.2 Energy Band Model for a Doped Semiconductor 62
 - 2.10.3 Compensated Semiconductors 62
- 2.11 Overview of Integrated Circuit Fabrication 64
 - Summary* 67
 - Key Terms* 68
 - Reference* 69
 - Additional Reading* 69
 - Important Equations* 69
 - Problems* 70

CHAPTER 3

SOLID-STATE DIODES AND DIODE CIRCUITS 74

- 3.1 The *pn* Junction Diode 75
 - 3.1.1 *pn* Junction Electrostatics 75
 - 3.1.2 Internal Diode Currents 79

- 3.2 The i - v Characteristics of the Diode 80
 - 3.3 The Diode Equation: A Mathematical Model for the Diode 82
 - 3.4 Diode Characteristics Under Reverse, Zero, and Forward Bias 85
 - 3.4.1 Reverse Bias 85
 - 3.4.2 Zero Bias 85
 - 3.4.3 Forward Bias 86
 - 3.5 Diode Temperature Coefficient 89
 - 3.6 Diodes Under Reverse Bias 89
 - 3.6.1 Saturation Current in Real Diodes 90
 - 3.6.2 Reverse Breakdown 91
 - 3.6.3 Diode Model for the Breakdown Region 92
 - 3.7 pn Junction Capacitance 92
 - 3.7.1 Reverse Bias 92
 - 3.7.2 Forward Bias 93
 - 3.8 Schottky Barrier Diode 93
 - 3.9 Diode SPICE Model and Layout 94
 - 3.10 Diode Circuit Analysis 96
 - 3.10.1 Load-Line Analysis 96
 - 3.10.2 Analysis Using the Mathematical Model for the Diode 98
 - 3.10.3 The Ideal Diode Model 102
 - 3.10.4 Constant Voltage Drop Model 104
 - 3.10.5 Model Comparison and Discussion 105
 - 3.11 Multiple-Diode Circuits 106
 - 3.12 Analysis of Diodes Operating in the Breakdown Region 109
 - 3.12.1 Load-Line Analysis 109
 - 3.12.2 Analysis with the Piecewise Linear Model 109
 - 3.12.3 Voltage Regulation 110
 - 3.12.4 Analysis Including Zener Resistance 111
 - 3.12.5 Line and Load Regulation 112
 - 3.13 Half-Wave Rectifier Circuits 113
 - 3.13.1 Half-Wave Rectifier with Resistor Load 113
 - 3.13.2 Rectifier Filter Capacitor 114
 - 3.13.3 Half-Wave Rectifier with RC Load 115
 - 3.13.4 Ripple Voltage and Conduction Interval 116
 - 3.13.5 Diode Current 118
 - 3.13.6 Surge Current 120
 - 3.13.7 Peak-Inverse-Voltage (PIV) Rating 120
 - 3.13.8 Diode Power Dissipation 120
 - 3.13.9 Half-Wave Rectifier with Negative Output Voltage 121
 - 3.14 Full-Wave Rectifier Circuits 123
 - 3.14.1 Full-Wave Rectifier with Negative Output Voltage 124
 - 3.15 Full-Wave Bridge Rectification 125
 - 3.16 Rectifier Comparison and Design Tradeoffs 125
 - 3.17 Dynamic Switching Behavior of the Diode 129
 - 3.18 Photo Diodes, Solar Cells, and Light-Emitting Diodes 130
 - 3.18.1 Photo Diodes and Photodetectors 130
 - 3.18.2 Power Generation from Solar Cells 131
 - 3.18.3 Light-Emitting Diodes (LEDs) 132
 - Summary* 133
 - Key Terms* 134
 - Reference* 135
 - Additional Reading* 135
 - Problems* 135
- CHAPTER 4**
- FIELD-EFFECT TRANSISTORS 145**
- 4.1 Characteristics of the MOS Capacitor 146
 - 4.1.1 Accumulation Region 147
 - 4.1.2 Depletion Region 148
 - 4.1.3 Inversion Region 148
 - 4.2 The NMOS Transistor 148
 - 4.2.1 Qualitative i - v Behavior of the NMOS Transistor 149
 - 4.2.2 Triode Region Characteristics of the NMOS Transistor 150
 - 4.2.3 On Resistance 153
 - 4.2.4 Saturation of the i - v Characteristics 154
 - 4.2.5 Mathematical Model in the Saturation (Pinch-Off) Region 155
 - 4.2.6 Transconductance 157
 - 4.2.7 Channel-Length Modulation 157
 - 4.2.8 Transfer Characteristics and Depletion-Mode MOSFETS 158
 - 4.2.9 Body Effect or Substrate Sensitivity 159
 - 4.3 PMOS Transistors 161
 - 4.4 MOSFET Circuit Symbols 163
 - 4.5 Capacitances in MOS Transistors 165
 - 4.5.1 NMOS Transistor Capacitances in the Triode Region 165
 - 4.5.2 Capacitances in the Saturation Region 166
 - 4.5.3 Capacitances in Cutoff 166
 - 4.6 MOSFET Modeling in SPICE 167

- 4.7 MOS Transistor Scaling 169
 - 4.7.1 Drain Current 169
 - 4.7.2 Gate Capacitance 169
 - 4.7.3 Circuit and Power Densities 170
 - 4.7.4 Power-Delay Product 170
 - 4.7.5 Cutoff Frequency 171
 - 4.7.6 High Field Limitations 171
 - 4.7.7 Subthreshold Conduction 172
 - 4.8 MOS Transistor Fabrication and Layout Design Rules 172
 - 4.8.1 Minimum Feature Size and Alignment Tolerance 173
 - 4.8.2 MOS Transistor Layout 173
 - 4.9 Biasing the NMOS Field-Effect Transistor 176
 - 4.9.1 Why Do We Need Bias? 176
 - 4.9.2 Constant Gate-Source Voltage Bias 178
 - 4.9.3 Load Line Analysis for the Q-Point 181
 - 4.9.4 Four-Resistor Biasing 182
 - 4.10 Biasing the PMOS Field-Effect Transistor 188
 - 4.11 The Junction Field-Effect Transistor (JFET) 190
 - 4.11.1 The JFET with Bias Applied 191
 - 4.11.2 JFET Channel with Drain-Source Bias 191
 - 4.11.3 n -Channel JFET i - v Characteristics 193
 - 4.11.4 The p -Channel JFET 195
 - 4.11.5 Circuit Symbols and JFET Model Summary 195
 - 4.11.6 JFET Capacitances 196
 - 4.12 JFET Modeling in SPICE 197
 - 4.13 Biasing the JFET and Depletion-Mode MOSFET 198
 - Summary* 200
 - Key Terms* 202
 - References* 203
 - Problems* 204
- CHAPTER 5**
- BIPOLAR JUNCTION TRANSISTORS 217**
- 5.1 Physical Structure of the Bipolar Transistor 218
 - 5.2 The Transport Model for the npn Transistor 219
 - 5.2.1 Forward Characteristics 220
 - 5.2.2 Reverse Characteristics 222
 - 5.2.3 The Complete Transport Model Equations for Arbitrary Bias Conditions 223
 - 5.3 The pnp Transistor 225
 - 5.4 Equivalent Circuit Representations for the Transport Models 227
 - 5.5 The i - v Characteristics of the Bipolar Transistor 228
 - 5.5.1 Output Characteristics 228
 - 5.5.2 Transfer Characteristics 229
 - 5.6 The Operating Regions of the Bipolar Transistor 230
 - 5.7 Transport Model Simplifications 231
 - 5.7.1 Simplified Model for the Cutoff Region 231
 - 5.7.2 Model Simplifications for the Forward-Active Region 233
 - 5.7.3 Diodes in Bipolar Integrated Circuits 239
 - 5.7.4 Simplified Model for the Reverse-Active Region 240
 - 5.7.5 Modeling Operation in the Saturation Region 242
 - 5.8 Nonideal Behavior of the Bipolar Transistor 245
 - 5.8.1 Junction Breakdown Voltages 246
 - 5.8.2 Minority-Carrier Transport in the Base Region 246
 - 5.8.3 Base Transit Time 247
 - 5.8.4 Diffusion Capacitance 249
 - 5.8.5 Frequency Dependence of the Common-Emitter Current Gain 250
 - 5.8.6 The Early Effect and Early Voltage 250
 - 5.8.7 Modeling the Early Effect 251
 - 5.8.8 Origin of the Early Effect 251
 - 5.9 Transconductance 252
 - 5.10 Bipolar Technology and SPICE Model 253
 - 5.10.1 Qualitative Description 253
 - 5.10.2 SPICE Model Equations 254
 - 5.10.3 High-Performance Bipolar Transistors 255
 - 5.11 Practical Bias Circuits for the BJT 256
 - 5.11.1 Four-Resistor Bias Network 258
 - 5.11.2 Design Objectives for the Four-Resistor Bias Network 260
 - 5.11.3 Iterative Analysis of the Four-Resistor Bias Circuit 266
 - 5.12 Tolerances in Bias Circuits 266
 - 5.12.1 Worst-Case Analysis 267
 - 5.12.2 Monte Carlo Analysis 269
- Summary* 272
- Key Terms* 274
- References* 274
- Problems* 275

PART TWO

DIGITAL ELECTRONICS 285

CHAPTER 6

INTRODUCTION TO DIGITAL ELECTRONICS 287

- 6.1 Ideal Logic Gates 289
- 6.2 Logic Level Definitions and Noise Margins 289
 - 6.2.1 Logic Voltage Levels 291
 - 6.2.2 Noise Margins 291
 - 6.2.3 Logic Gate Design Goals 292
- 6.3 Dynamic Response of Logic Gates 293
 - 6.3.1 Rise Time and Fall Time 293
 - 6.3.2 Propagation Delay 294
 - 6.3.3 Power-Delay Product 294
- 6.4 Review of Boolean Algebra 295
- 6.5 NMOS Logic Design 297
 - 6.5.1 NMOS Inverter with Resistive Load 298
 - 6.5.2 Design of the W/L Ratio of M_S 299
 - 6.5.3 Load Resistor Design 300
 - 6.5.4 Load-Line Visualization 300
 - 6.5.5 On-Resistance of the Switching Device 302
 - 6.5.6 Noise Margin Analysis 303
 - 6.5.7 Calculation of V_{IL} and V_{OH} 303
 - 6.5.8 Calculation of V_{IH} and V_{OL} 304
 - 6.5.9 Load Resistor Problems 305
- 6.6 Transistor Alternatives to the Load Resistor 306
 - 6.6.1 The NMOS Saturated Load Inverter 307
 - 6.6.2 NMOS Inverter with a Linear Load Device 315
 - 6.6.3 NMOS Inverter with a Depletion-Mode Load 316
 - 6.6.4 Static Design of the Pseudo NMOS Inverter 319
- 6.7 NMOS Inverter Summary and Comparison 323
- 6.8 NMOS NAND and NOR Gates 324
 - 6.8.1 NOR Gates 325
 - 6.8.2 NAND Gates 326
 - 6.8.3 NOR and NAND Gate Layouts in NMOS Depletion-Mode Technology 327
- 6.9 Complex NMOS Logic Design 328
- 6.10 Power Dissipation 333
 - 6.10.1 Static Power Dissipation 333
 - 6.10.2 Dynamic Power Dissipation 334
 - 6.10.3 Power Scaling in MOS Logic Gates 335
- 6.11 Dynamic Behavior of MOS Logic Gates 337
 - 6.11.1 Capacitances in Logic Circuits 337
 - 6.11.2 Dynamic Response of the NMOS Inverter with a Resistive Load 338
 - 6.11.3 Pseudo NMOS Inverter 343
 - 6.11.4 A Final Comparison of NMOS Inverter Delays 344
 - 6.11.5 Scaling Based Upon Reference Circuit Simulation 346
 - 6.11.6 Ring Oscillator Measurement of Intrinsic Gate Delay 346
 - 6.11.7 Unloaded Inverter Delay 347
- 6.12 PMOS Logic 349
 - 6.12.1 PMOS Inverters 349
 - 6.12.2 NOR and NAND Gates 352

Summary 352
Key Terms 354
References 355
Additional Reading 355
Problems 355

CHAPTER 7

COMPLEMENTARY MOS (CMOS) LOGIC DESIGN 367

- 7.1 CMOS Inverter Technology 368
 - 7.1.1 CMOS Inverter Layout 370
- 7.2 Static Characteristics of the CMOS Inverter 370
 - 7.2.1 CMOS Voltage Transfer Characteristics 371
 - 7.2.2 Noise Margins for the CMOS Inverter 373
- 7.3 Dynamic Behavior of the CMOS Inverter 375
 - 7.3.1 Propagation Delay Estimate 375
 - 7.3.2 Rise and Fall Times 377
 - 7.3.3 Performance Scaling 377
 - 7.3.4 Delay of Cascaded Inverters 379
- 7.4 Power Dissipation and Power Delay Product in CMOS 380
 - 7.4.1 Static Power Dissipation 380
 - 7.4.2 Dynamic Power Dissipation 381
 - 7.4.3 Power-Delay Product 382
- 7.5 CMOS NOR and NAND Gates 384
 - 7.5.1 CMOS NOR Gate 384
 - 7.5.2 CMOS NAND Gates 387
- 7.6 Design of Complex Gates in CMOS 388
- 7.7 Minimum Size Gate Design and Performance 393
- 7.8 Dynamic Domino CMOS Logic 395
- 7.9 Cascade Buffers 397
 - 7.9.1 Cascade Buffer Delay Model 397
 - 7.9.2 Optimum Number of Stages 398
- 7.10 The CMOS Transmission Gate 400
- 7.11 CMOS Latchup 401

Summary 404
 Key Terms 405
 References 406
 Problems 406

CHAPTER 8

MOS MEMORY AND STORAGE CIRCUITS 416

- 8.1 Random Access Memory 417
 - 8.1.1 Random Access Memory (RAM) Architecture 417
 - 8.1.2 A 256-Mb Memory Chip 418
 - 8.2 Static Memory Cells 419
 - 8.2.1 Memory Cell Isolation and Access—The 6-T Cell 422
 - 8.2.2 The Read Operation 422
 - 8.2.3 Writing Data into the 6-T Cell 426
 - 8.3 Dynamic Memory Cells 428
 - 8.3.1 The One-Transistor Cell 430
 - 8.3.2 Data Storage in the 1-T Cell 430
 - 8.3.3 Reading Data from the 1-T Cell 431
 - 8.3.4 The Four-Transistor Cell 433
 - 8.4 Sense Amplifiers 434
 - 8.4.1 A Sense Amplifier for the 6-T Cell 434
 - 8.4.2 A Sense Amplifier for the 1-T Cell 436
 - 8.4.3 The Boosted Wordline Circuit 438
 - 8.4.4 Clocked CMOS Sense Amplifiers 438
 - 8.5 Address Decoders 440
 - 8.5.1 NOR Decoder 440
 - 8.5.2 NAND Decoder 440
 - 8.5.3 Decoders in Domino CMOS Logic 443
 - 8.5.4 Pass-Transistor Column Decoder 443
 - 8.6 Read-Only Memory (ROM) 444
 - 8.7 Flip-Flops 447
 - 8.7.1 RS Flip-Flop 449
 - 8.7.2 The D-Latch Using Transmission Gates 450
 - 8.7.3 A Master-Slave D Flip-Flop 450
- Summary 451
 Key Terms 452
 References 452
 Problems 453

CHAPTER 9

BIPOLAR LOGIC CIRCUITS 460

- 9.1 The Current Switch (Emitter-Coupled Pair) 461
 - 9.1.1 Mathematical Model for Static Behavior of the Current Switch 462

- 9.1.2 Current Switch Analysis for $v_I > V_{REF}$ 463
- 9.1.3 Current Switch Analysis for $v_I < V_{REF}$ 464
- 9.2 The Emitter-Coupled Logic (ECL) Gate 464
 - 9.2.1 ECL Gate with $v_I = V_H$ 465
 - 9.2.2 ECL Gate with $v_I = V_L$ 466
 - 9.2.3 Input Current of the ECL Gate 466
 - 9.2.4 ECL Summary 466
- 9.3 Noise Margin Analysis for the ECL Gate 467
 - 9.3.1 V_{IL} , V_{OH} , V_{IH} , and V_{OL} 467
 - 9.3.2 Noise Margins 468
- 9.4 Current Source Implementation 469
- 9.5 The ECL OR-NOR Gate 471
- 9.6 The Emitter Follower 473
 - 9.6.1 Emitter Follower with a Load Resistor 474
- 9.7 “Emitter Dotting” or “Wired-OR” Logic 476
 - 9.7.1 Parallel Connection of Emitter-Follower Outputs 477
 - 9.7.2 The Wired-OR Logic Function 477
- 9.8 ECL Power-Delay Characteristics 477
 - 9.8.1 Power Dissipation 477
 - 9.8.2 Gate Delay 479
 - 9.8.3 Power-Delay Product 480
- 9.9 Current Mode Logic 481
 - 9.9.1 CML Logic Gates 481
 - 9.9.2 CML Logic Levels 482
 - 9.9.3 V_{EE} Supply Voltage 482
 - 9.9.4 Higher-Level CML 483
 - 9.9.5 CML Power Reduction 484
 - 9.9.6 NMOS CML 485
- 9.10 The Saturating Bipolar Inverter 487
 - 9.10.1 Static Inverter Characteristics 488
 - 9.10.2 Saturation Voltage of the Bipolar Transistor 488
 - 9.10.3 Load-Line Visualization 491
 - 9.10.4 Switching Characteristics of the Saturated BJT 491
- 9.11 A Transistor-Transistor Logic (TTL) Prototype 494
 - 9.11.1 TTL Inverter for $v_I = V_L$ 494
 - 9.11.2 TTL Inverter for $v_I = V_H$ 495
 - 9.11.3 Power in the Prototype TTL Gate 496
 - 9.11.4 V_{IH} , V_{IL} , and Noise Margins for the TTL Prototype 496
 - 9.11.5 Prototype Inverter Summary 498
 - 9.11.6 Fanout Limitations of the TTL Prototype 498
- 9.12 The Standard 7400 Series TTL Inverter 500
 - 9.12.1 Analysis for $v_I = V_L$ 500
 - 9.12.2 Analysis for $v_I = V_H$ 501

- 9.12.3 Power Consumption 503
- 9.12.4 TTL Propagation Delay and Power-Delay Product 503
- 9.12.5 TTL Voltage Transfer Characteristic and Noise Margins 503
- 9.12.6 Fanout Limitations of Standard TTL 504
- 9.13 Logic Functions in TTL 504
 - 9.13.1 Multi-Emitter Input Transistors 505
 - 9.13.2 TTL NAND Gates 505
 - 9.13.3 Input Clamping Diodes 506
- 9.14 Schottky-Clamped TTL 506
- 9.15 Comparison of the Power-Delay Products of ECL and TTL 508
- 9.16 BiCMOS Logic 508
 - 9.16.1 BiCMOS Buffers 509
 - 9.16.2 BiNMOS Inverters 511
 - 9.16.3 BiCMOS Logic Gates 513

Summary 513
Key Terms 515
References 515
Additional Reading 515
Problems 516
- 10.9 Analysis of Circuits Containing Ideal Operational Amplifiers 552
 - 10.9.1 The Inverting Amplifier 553
 - 10.9.2 The Transresistance Amplifier—A Current-to-Voltage Converter 556
 - 10.9.3 The Noninverting Amplifier 558
 - 10.9.4 The Unity-Gain Buffer, or Voltage Follower 561
 - 10.9.5 The Summing Amplifier 563
 - 10.9.6 The Difference Amplifier 565
- 10.10 Frequency-Dependent Feedback 568
 - 10.10.1 Bode Plots 568
 - 10.10.2 The Low-Pass Amplifier 568
 - 10.10.3 The High-Pass Amplifier 572
 - 10.10.4 Band-Pass Amplifiers 575
 - 10.10.5 An Active Low-Pass Filter 578
 - 10.10.6 An Active High-Pass Filter 581
 - 10.10.7 The Integrator 582
 - 10.10.8 The Differentiator 586

Summary 586
Key Terms 588
References 588
Additional Reading 589
Problems 589

PART THREE

ANALOG ELECTRONICS 527

CHAPTER 10

ANALOG SYSTEMS AND IDEAL OPERATIONAL AMPLIFIERS 529

- 10.1 An Example of an Analog Electronic System 530
- 10.2 Amplification 531
 - 10.2.1 Voltage Gain 532
 - 10.2.2 Current Gain 533
 - 10.2.3 Power Gain 533
 - 10.2.4 The Decibel Scale 534
- 10.3 Two-Port Models for Amplifiers 537
 - 10.3.1 The g -parameters 537
- 10.4 Mismatched Source and Load Resistances 541
- 10.5 Introduction to Operational Amplifiers 544
 - 10.5.1 The Differential Amplifier 544
 - 10.5.2 Differential Amplifier Voltage Transfer Characteristic 545
 - 10.5.3 Voltage Gain 545
- 10.6 Distortion in Amplifiers 548
- 10.7 Differential Amplifier Model 549
- 10.8 Ideal Differential and Operational Amplifiers 551
 - 10.8.1 Assumptions for Ideal Operational Amplifier Analysis 551

CHAPTER 11

NONIDEAL OPERATIONAL AMPLIFIERS AND FEEDBACK AMPLIFIER STABILITY 600

- 11.1 Classic Feedback Systems 601
 - 11.1.1 Closed-Loop Gain Analysis 602
 - 11.1.2 Gain Error 602
- 11.2 Analysis of Circuits Containing Nonideal Operational Amplifiers 603
 - 11.2.1 Finite Open-Loop Gain 603
 - 11.2.2 Nonzero Output Resistance 606
 - 11.2.3 Finite Input Resistance 610
 - 11.2.4 Summary of Nonideal Inverting and Noninverting Amplifiers 614
- 11.3 Series and Shunt Feedback Circuits 615
 - 11.3.1 Feedback Amplifier Categories 615
 - 11.3.2 Voltage Amplifiers—Series-Shunt Feedback 616
 - 11.3.3 Transimpedance Amplifiers—Shunt-Shunt Feedback 616
 - 11.3.4 Current Amplifiers—Shunt-Series Feedback 616
 - 11.3.5 Transconductance Amplifiers—Series-Series Feedback 616
- 11.4 Unified Approach to Feedback Amplifier Gain Calculation 616

- 11.4.1 Closed-Loop Gain Analysis 617
 - 11.4.2 Resistance Calculation Using Blackman'S Theorem 617
 - 11.5 Series-Shunt Feedback—Voltage Amplifiers 617
 - 11.5.1 Closed-Loop Gain Calculation 618
 - 11.5.2 Input Resistance Calculation 618
 - 11.5.3 Output Resistance Calculation 619
 - 11.5.4 Series-Shunt Feedback Amplifier Summary 620
 - 11.6 Shunt-Shunt Feedback—Transresistance Amplifiers 624
 - 11.6.1 Closed-Loop Gain Calculation 625
 - 11.6.2 Input Resistance Calculation 625
 - 11.6.3 Output Resistance Calculation 625
 - 11.6.4 Shunt-Shunt Feedback Amplifier Summary 626
 - 11.7 Series-Series Feedback—Transconductance Amplifiers 629
 - 11.7.1 Closed-Loop Gain Calculation 630
 - 11.7.2 Input Resistance Calculation 630
 - 11.7.3 Output Resistance Calculation 631
 - 11.7.4 Series-Series Feedback Amplifier Summary 631
 - 11.8 Shunt-Series Feedback—Current Amplifiers 633
 - 11.8.1 Closed-Loop Gain Calculation 634
 - 11.8.2 Input Resistance Calculation 635
 - 11.8.3 Output Resistance Calculation 635
 - 11.8.4 Series-Series Feedback Amplifier Summary 635
 - 11.9 Finding the Loop Gain Using Successive Voltage and Current Injection 638
 - 11.9.1 Simplifications 641
 - 11.10 Distortion Reduction Through the Use of Feedback 641
 - 11.11 DC Error Sources and Output Range Limitations 642
 - 11.11.1 Input-Offset Voltage 643
 - 11.11.2 Offset-Voltage Adjustment 644
 - 11.11.3 Input-Bias and Offset Currents 645
 - 11.11.4 Output Voltage and Current Limits 647
 - 11.12 Common-Mode Rejection and Input Resistance 650
 - 11.12.1 Finite Common-Mode Rejection Ratio 650
 - 11.12.2 Why Is CMRR Important? 651
 - 11.12.3 Voltage-Follower Gain Error Due to CMRR 654
 - 11.12.4 Common-Mode Input Resistance 656
 - 11.12.5 An Alternate Interpretation of CMRR 657
 - 11.12.6 Power Supply Rejection Ratio 657
 - 11.13 Frequency Response and Bandwidth of Operational Amplifiers 659
 - 11.13.1 Frequency Response of the Noninverting Amplifier 661
 - 11.13.2 Inverting Amplifier Frequency Response 664
 - 11.13.3 Using Feedback to Control Frequency Response 666
 - 11.13.4 Large-Signal Limitations—Slew Rate and Full-Power Bandwidth 668
 - 11.13.5 Macro Model for Operational Amplifier Frequency Response 669
 - 11.13.6 Complete Op Amp Macro Models in SPICE 670
 - 11.13.7 Examples of Commercial General-Purpose Operational Amplifiers 670
 - 11.14 Stability of Feedback Amplifiers 671
 - 11.14.1 The Nyquist Plot 671
 - 11.14.2 First-Order Systems 672
 - 11.14.3 Second-Order Systems and Phase Margin 673
 - 11.14.4 Step Response and Phase Margin 674
 - 11.14.5 Third-Order Systems and Gain Margin 677
 - 11.14.6 Determining Stability from the Bode Plot 678

Summary 682
Key Terms 684
References 684
Problems 685
- CHAPTER 12**
- OPERATIONAL AMPLIFIER APPLICATIONS 697**
- 12.1 Cascaded Amplifiers 698
 - 12.1.1 Two-Port Representations 698
 - 12.1.2 Amplifier Terminology Review 700
 - 12.1.3 Frequency Response of Cascaded Amplifiers 703
 - 12.2 The Instrumentation Amplifier 711
 - 12.3 Active Filters 714
 - 12.3.1 Low-Pass Filter 714
 - 12.3.2 A High-Pass Filter with Gain 718
 - 12.3.3 Band-Pass Filter 720
 - 12.3.4 The Tow-Thomas Biquad 722
 - 12.3.5 Sensitivity 726
 - 12.3.6 Magnitude and Frequency Scaling 727

- 12.4 Switched-Capacitor Circuits 728
 - 12.4.1 A Switched-Capacitor Integrator 728
 - 12.4.2 Noninverting SC Integrator 730
 - 12.4.3 Switched-Capacitor Filters 732
 - 12.5 Digital-to-Analog Conversion 733
 - 12.5.1 D/A Converter Fundamentals 733
 - 12.5.2 D/A Converter Errors 734
 - 12.5.3 Digital-to-Analog Converter Circuits 737
 - 12.6 Analog-to-Digital Conversion 740
 - 12.6.1 A/D Converter Fundamentals 741
 - 12.6.2 Analog-to-Digital Converter Errors 742
 - 12.6.3 Basic A/D Conversion Techniques 743
 - 12.7 Oscillators 754
 - 12.7.1 The Barkhausen Criteria for Oscillation 754
 - 12.7.2 Oscillators Employing Frequency-Selective RC Networks 755
 - 12.8 Nonlinear Circuit Applications 760
 - 12.8.1 A Precision Half-Wave Rectifier 760
 - 12.8.2 Nonsaturating Precision-Rectifier Circuit 761
 - 12.9 Circuits Using Positive Feedback 763
 - 12.9.1 The Comparator and Schmitt Trigger 763
 - 12.9.2 The Astable Multivibrator 765
 - 12.9.3 The Monostable Multivibrator or One Shot 766
 - Summary* 770
 - Key Terms* 772
 - Additional Reading* 773
 - Problems* 773
- CHAPTER 13**
- SMALL-SIGNAL MODELING AND LINEAR AMPLIFICATION 786**
- 13.1 The Transistor as an Amplifier 787
 - 13.1.1 The BJT Amplifier 788
 - 13.1.2 The MOSFET Amplifier 789
 - 13.2 Coupling and Bypass Capacitors 790
 - 13.3 Circuit Analysis Using dc and ac Equivalent Circuits 792
 - 13.3.1 Menu for dc and ac Analysis 792
 - 13.4 Introduction to Small-Signal Modeling 796
 - 13.4.1 Graphical Interpretation of the Small-Signal Behavior of the Diode 796
 - 13.4.2 Small-Signal Modeling of the Diode 797
 - 13.5 Small-Signal Models for Bipolar Junction Transistors 799
 - 13.5.1 The Hybrid-Pi Model 801
 - 13.5.2 Graphical Interpretation of the Transconductance 802
 - 13.5.3 Small-Signal Current Gain 802
 - 13.5.4 The Intrinsic Voltage Gain of the BJT 803
 - 13.5.5 Equivalent Forms of the Small-Signal Model 804
 - 13.5.6 Simplified Hybrid Pi Model 805
 - 13.5.7 Definition of a Small Signal for the Bipolar Transistor 805
 - 13.5.8 Small-Signal Model for the *pnp* Transistor 807
 - 13.5.9 ac Analysis Versus Transient Analysis in SPICE 807
 - 13.6 The Common-Emitter (C-E) Amplifier 808
 - 13.6.1 Terminal Voltage Gain 809
 - 13.6.2 Input Resistance 809
 - 13.6.3 Signal Source Voltage Gain 810
 - 13.7 Important Limits and Model Simplifications 810
 - 13.7.1 A Design Guide for the Common-Emitter Amplifier 810
 - 13.7.2 Upper Bound on the Common-Emitter Gain 812
 - 13.7.3 Small-Signal Limit for the Common-emitter Amplifier 812
 - 13.8 Small-Signal Models for Field-Effect Transistors 815
 - 13.8.1 Small-Signal Model for the MOSFET 815
 - 13.8.2 Intrinsic Voltage Gain of the MOSFET 817
 - 13.8.3 Definition of Small-Signal Operation for the MOSFET 817
 - 13.8.4 Body Effect in the Four-Terminal MOSFET 818
 - 13.8.5 Small-Signal Model for the PMOS Transistor 819
 - 13.8.6 Small-Signal Model for the Junction Field-Effect Transistor 820
 - 13.9 Summary and Comparison of the Small-Signal Models of the BJT and FET 821
 - 13.10 The Common-Source Amplifier 824
 - 13.10.1 Common-Source Terminal Voltage Gain 825
 - 13.10.2 Signal Source Voltage Gain for the Common-Source Amplifier 825
 - 13.10.3 A Design Guide for the Common-Source Amplifier 826
 - 13.10.4 Small-Signal Limit for the Common-Source Amplifier 827

- 13.10.5 Input Resistances of the Common-Emitter and Common-Source Amplifiers 829
 - 13.10.6 Common-Emitter and Common-Source Output Resistances 832
 - 13.10.7 Comparison of the Three Amplifier Resistances 838
 - 13.11 Common-Emitter and Common-Source Amplifier Summary 838
 - 13.11.1 Guidelines for Neglecting the Transistor Output Resistance 839
 - 13.12 Amplifier Power and Signal Range 839
 - 13.12.1 Power Dissipation 839
 - 13.12.2 Signal Range 840

Summary 843
Key Terms 844
Problems 845
- CHAPTER 14**
SINGLE-TRANSISTOR AMPLIFIERS 857
- 14.1 Amplifier Classification 858
 - 14.1.1 Signal Injection and Extraction—The BJT 858
 - 14.1.2 Signal Injection and Extraction—The FET 859
 - 14.1.3 Common-Emitter (C-E) and Common-Source (C-S) Amplifiers 860
 - 14.1.4 Common-Collector (C-C) and Common-Drain (C-D) Topologies 861
 - 14.1.5 Common-Base (C-B) and Common-Gate (C-G) Amplifiers 863
 - 14.1.6 Small-Signal Model Review 864
 - 14.2 Inverting Amplifiers—Common-Emitter and Common-Source Circuits 864
 - 14.2.1 The Common-Emitter (C-E) Amplifier 864
 - 14.2.2 Common-Emitter Example Comparison 877
 - 14.2.3 The Common-Source Amplifier 877
 - 14.2.4 Small-Signal Limit for the Common-Source Amplifier 880
 - 14.2.5 Common-Emitter and Common-Source Amplifier Characteristics 884
 - 14.2.6 C-E/C-S Amplifier Summary 885
 - 14.2.7 Equivalent Transistor Representation of the Generalized C-E/C-S Transistor 885
 - 14.3 Follower Circuits—Common-Collector and Common-Drain Amplifiers 886
 - 14.3.1 Terminal Voltage Gain 886
 - 14.3.2 Input Resistance 887
 - 14.3.3 Signal Source Voltage Gain 888
 - 14.3.4 Follower Signal Range 888
 - 14.3.5 Follower Output Resistance 889
 - 14.3.6 Current Gain 890
 - 14.3.7 C-C/C-D Amplifier Summary 890
 - 14.4 Noninverting Amplifiers—Common-Base and Common-Gate Circuits 894
 - 14.4.1 Terminal Voltage Gain and Input Resistance 895
 - 14.4.2 Signal Source Voltage Gain 896
 - 14.4.3 Input Signal Range 897
 - 14.4.4 Resistance at the Collector and Drain Terminals 897
 - 14.4.5 Current Gain 898
 - 14.4.6 Overall Input and Output Resistances for the Noninverting Amplifiers 899
 - 14.4.7 C-B/C-G Amplifier Summary 902
 - 14.5 Amplifier Prototype Review and Comparison 903
 - 14.5.1 The BJT Amplifiers 903
 - 14.5.2 The FET Amplifiers 905
 - 14.6 Common-Source Amplifiers Using MOS Inverters 907
 - 14.6.1 Voltage Gain Estimate 908
 - 14.6.2 Detailed Analysis 909
 - 14.6.3 Alternative Loads 910
 - 14.6.4 Input and Output Resistances 911
 - 14.7 Coupling and Bypass Capacitor Design 914
 - 14.7.1 Common-Emitter and Common-Source Amplifiers 914
 - 14.7.2 Common-Collector and Common-Drain Amplifiers 919
 - 14.7.3 Common-Base and Common-Gate Amplifiers 921
 - 14.7.4 Setting Lower Cutoff Frequency f_L 924
 - 14.8 Amplifier Design Examples 925
 - 14.8.1 Monte Carlo Evaluation of the Common-Base Amplifier Design 934
 - 14.9 Multistage ac-Coupled Amplifiers 939
 - 14.9.1 A Three-Stage ac-Coupled Amplifier 939
 - 14.9.2 Voltage Gain 941
 - 14.9.3 Input Resistance 943
 - 14.9.4 Signal Source Voltage Gain 943
 - 14.9.5 Output Resistance 943
 - 14.9.6 Current and Power Gain 944

- 14.9.7 Input Signal Range 945
- 14.9.8 Estimating the Lower Cutoff Frequency of the Multistage Amplifier 948

Summary 950

Key Terms 951

Additional Reading 952

Problems 952

CHAPTER 15

DIFFERENTIAL AMPLIFIERS AND OPERATIONAL AMPLIFIER DESIGN 968

- 15.1 Differential Amplifiers 969
 - 15.1.1 Bipolar and MOS Differential Amplifiers 969
 - 15.1.2 dc Analysis of the Bipolar Differential Amplifier 970
 - 15.1.3 Transfer Characteristic for the Bipolar Differential Amplifier 972
 - 15.1.4 ac Analysis of the Bipolar Differential Amplifier 973
 - 15.1.5 Differential-Mode Gain and Input and Output Resistances 974
 - 15.1.6 Common-Mode Gain and Input Resistance 976
 - 15.1.7 Common-Mode Rejection Ratio (CMRR) 978
 - 15.1.8 Analysis Using Differential- and Common-Mode Half-Circuits 979
 - 15.1.9 Biasing with Electronic Current Sources 982
 - 15.1.10 Modeling the Electronic Current Source in SPICE 983
 - 15.1.11 dc Analysis of the MOSFET Differential Amplifier 983
 - 15.1.12 Differential-Mode Input Signals 985
 - 15.1.13 Small-Signal Transfer Characteristic for the MOS Differential Amplifier 986
 - 15.1.14 Common-Mode Input Signals 986
 - 15.1.15 Two-Port Model for Differential Pairs 987
- 15.2 Evolution to Basic Operational Amplifiers 991
 - 15.2.1 A Two-Stage Prototype for an Operational Amplifier 992
 - 15.2.2 Improving the Op Amp Voltage Gain 997
 - 15.2.3 Output Resistance Reduction 998
 - 15.2.4 A CMOS Operational Amplifier Prototype 1002

- 15.2.5 BiCMOS Amplifiers 1004

15.2.6 All Transistor Implementations 1004

15.3 Output Stages 1006

15.3.1 The Source Follower—A Class-A Output Stage 1006

15.3.2 Efficiency of Class-A Amplifiers 1007

15.3.3 Class-B Push-Pull Output Stage 1008

15.3.4 Class-AB Amplifiers 1010

15.3.5 Class-AB Output Stages for Operational Amplifiers 1011

15.3.6 Short-Circuit Protection 1011

15.3.7 Transformer Coupling 1013

15.4 Electronic Current Sources 1016

15.4.1 Single-Transistor Current Sources 1017

15.4.2 Figure of Merit for Current Sources 1017

15.4.3 Higher Output Resistance Sources 1018

15.4.4 Current Source Design Examples 1018

Summary 1027

Key Terms 1028

References 1029

Additional Reading 1029

Problems 1029

CHAPTER 16

ANALOG INTEGRATED CIRCUIT DESIGN TECHNIQUES 1046

- 16.1 Circuit Element Matching 1047
- 16.2 Current Mirrors 1049
 - 16.2.1 dc Analysis of the MOS Transistor Current Mirror 1049
 - 16.2.2 Changing the MOS Mirror Ratio 1051
 - 16.2.3 dc Analysis of the Bipolar Transistor Current Mirror 1052
 - 16.2.4 Altering the BJT Current Mirror Ratio 1054
 - 16.2.5 Multiple Current Sources 1055
 - 16.2.6 Buffered Current Mirror 1056
 - 16.2.7 Output Resistance of the Current Mirrors 1057
 - 16.2.8 Two-Port Model for the Current Mirror 1058
 - 16.2.9 The Widlar Current Source 1060
 - 16.2.10 The MOS Version of the Widlar Source 1063

- 16.3 High-Output-Resistance Current Mirrors 1063
 - 16.3.1 The Wilson Current Sources 1064
 - 16.3.2 Output Resistance of the Wilson Source 1065
 - 16.3.3 Cascode Current Sources 1066
 - 16.3.4 Output Resistance of the Cascode Sources 1067
 - 16.3.5 Regulated Cascode Current Source 1068
 - 16.3.6 Current Mirror Summary 1069
 - 16.4 Reference Current Generation 1072
 - 16.5 Supply-Independent Biasing 1073
 - 16.5.1 A V_{BE} -Based Reference 1073
 - 16.5.2 The Widlar Source 1073
 - 16.5.3 Power-Supply-Independent Bias Cell 1074
 - 16.5.4 A Supply-Independent MOS Reference Cell 1075
 - 16.6 The Bandgap Reference 1077
 - 16.7 The Current Mirror As an Active Load 1081
 - 16.7.1 CMOS Differential Amplifier with Active Load 1081
 - 16.7.2 Bipolar Differential Amplifier with Active Load 1088
 - 16.8 Active Loads in Operational Amplifiers 1092
 - 16.8.1 CMOS Op Amp Voltage Gain 1092
 - 16.8.2 dc Design Considerations 1093
 - 16.8.3 Bipolar Operational Amplifiers 1095
 - 16.8.4 Input Stage Breakdown 1096
 - 16.9 The $\mu A741$ Operational Amplifier 1097
 - 16.9.1 Overall Circuit Operation 1097
 - 16.9.2 Bias Circuitry 1098
 - 16.9.3 dc Analysis of the 741 Input Stage 1099
 - 16.9.4 ac Analysis of the 741 Input Stage 1102
 - 16.9.5 Voltage Gain of the Complete Amplifier 1103
 - 16.9.6 The 741 Output Stage 1107
 - 16.9.7 Output Resistance 1109
 - 16.9.8 Short Circuit Protection 1109
 - 16.9.9 Summary of the $\mu A741$ Operational Amplifier Characteristics 1109
 - 16.10 The Gilbert Analog Multiplier 1110
 - Summary* 1112
 - Key Terms* 1113
 - References* 1114
 - Problems* 1114
-
- CHAPTER 17**
 - AMPLIFIER FREQUENCY RESPONSE 1128**
 - 17.1 Amplifier Frequency Response 1129
 - 17.1.1 Low-Frequency Response 1130
 - 17.1.2 Estimating ω_L in the Absence of a Dominant Pole 1130
 - 17.1.3 High-Frequency Response 1133
 - 17.1.4 Estimating ω_H in the Absence of a Dominant Pole 1133
 - 17.2 Direct Determination of the Low-Frequency Poles and Zeros—The Common-Source Amplifier 1134
 - 17.3 Estimation of ω_L Using the Short-Circuit Time-Constant Method 1139
 - 17.3.1 Estimate of ω_L for the Common-Emitter Amplifier 1140
 - 17.3.2 Estimate of ω_L for the Common-Source Amplifier 1144
 - 17.3.3 Estimate of ω_L for the Common-Base Amplifier 1145
 - 17.3.4 Estimate of ω_L for the Common-Gate Amplifier 1146
 - 17.3.5 Estimate of ω_L for the Common-Collector Amplifier 1147
 - 17.3.6 Estimate of ω_L for the Common-Drain Amplifier 1147
 - 17.4 Transistor Models at High Frequencies 1148
 - 17.4.1 Frequency-Dependent Hybrid-Pi Model for the Bipolar Transistor 1148
 - 17.4.2 Modeling C_π and C_μ in SPICE 1149
 - 17.4.3 Unity-Gain Frequency f_T 1149
 - 17.4.4 High-Frequency Model for the FET 1152
 - 17.4.5 Modeling C_{GS} and C_{GD} in SPICE 1153
 - 17.4.6 Channel Length Dependence of f_T 1153
 - 17.4.7 Limitations of the High-Frequency Models 1155
 - 17.5 Base Resistance in the Hybrid-Pi Model 1155
 - 17.5.1 Effect of Base Resistance on Midband Amplifiers 1156
 - 17.6 High-Frequency Common-Emitter and Common-Source Amplifier Analysis 1158
 - 17.6.1 The Miller Effect 1159
 - 17.6.2 Common-Emitter and Common-Source Amplifier High-Frequency Response 1160
 - 17.6.3 Direct Analysis of the Common-Emitter Transfer Characteristic 1162

| | | |
|---------|--|------|
| 17.6.4 | Poles of the Common-Emitter Amplifier | 1163 |
| 17.6.5 | Dominant Pole for the Common-Source Amplifier | 1166 |
| 17.6.6 | Estimation of ω_H Using the Open-Circuit Time-Constant Method | 1167 |
| 17.6.7 | Common-Source Amplifier with Source Degeneration Resistance | 1170 |
| 17.6.8 | Poles of the Common-Emitter with Emitter Degeneration Resistance | 1172 |
| 17.7 | Common-Base and Common-Gate Amplifier High-Frequency Response | 1174 |
| 17.8 | Common-Collector and Common-Drain Amplifier High-Frequency Response | 1177 |
| 17.9 | Single-Stage Amplifier High-Frequency Response Summary | 1179 |
| 17.9.1 | Amplifier Gain-Bandwidth Limitations | 1180 |
| 17.10 | Frequency Response of Multistage Amplifiers | 1181 |
| 17.10.1 | Differential Amplifier | 1181 |
| 17.10.2 | The Common-Collector/ Common-Base Cascade | 1182 |
| 17.10.3 | High-Frequency Response of the Cascode Amplifier | 1184 |
| 17.10.4 | Cutoff Frequency for the Current Mirror | 1185 |
| 17.10.5 | Three-Stage Amplifier Example | 1187 |
| 17.11 | Introduction to Radio Frequency Circuits | 1193 |
| 17.11.1 | Radio Frequency Amplifiers | 1194 |
| 17.11.2 | The Shunt-Peaked Amplifier | 1194 |
| 17.11.3 | Single-Tuned Amplifier | 1197 |
| 17.11.4 | Use of a Tapped Inductor—The Auto Transformer | 1199 |
| 17.11.5 | Multiple Tuned Circuits—Synchronous and Stagger Tuning | 1201 |
| 17.11.6 | Common-Source Amplifier with Inductive Degeneration | 1202 |
| 17.12 | Mixers and Balanced Modulators | 1205 |
| 17.12.1 | Introduction to Mixer Operation | 1205 |
| 17.12.2 | A Single-Balanced Mixer | 1206 |
| 17.12.3 | The Differential Pair as a Single-Balanced Mixer | 1207 |
| 17.12.4 | A Double-Balanced Mixer | 1208 |
| 17.12.5 | The Gilbert Multiplier as a Double-Balanced Mixer/Modulator | 1210 |

Summary 1213

Key Terms 1215

Reference 1215

Problems 1215

CHAPTER 18

TRANSISTOR FEEDBACK AMPLIFIERS AND OSCILLATORS 1228

| | | |
|--------|--|------|
| 18.1 | Basic Feedback System Review | 1229 |
| 18.1.1 | Closed-Loop Gain | 1229 |
| 18.1.2 | Closed-Loop Impedances | 1230 |
| 18.1.3 | Feedback Effects | 1230 |
| 18.2 | Feedback Amplifier Analysis at Midband | 1232 |
| 18.3 | Feedback Amplifier Circuit Examples | 1234 |
| 18.3.1 | Series-Shunt Feedback—Voltage Amplifiers | 1234 |
| 18.3.2 | Differential Input Series-Shunt Voltage Amplifier | 1239 |
| 18.3.3 | Shunt-Shunt Feedback—Transresistance Amplifiers | 1242 |
| 18.3.4 | Series-Series Feedback—Transconductance Amplifiers | 1248 |
| 18.3.5 | Shunt-Series Feedback—Current Amplifiers | 1251 |
| 18.4 | Review of Feedback Amplifier Stability | 1254 |
| 18.4.1 | Closed-Loop Response of the Uncompensated Amplifier | 1254 |
| 18.4.2 | Phase Margin | 1256 |
| 18.4.3 | Higher-Order Effects | 1259 |
| 18.4.4 | Response of the Compensated Amplifier | 1260 |
| 18.4.5 | Small-Signal Limitations | 1262 |
| 18.5 | Single-Pole Operational Amplifier Compensation | 1262 |
| 18.5.1 | Three-Stage Op Amp Analysis | 1263 |
| 18.5.2 | Transmission Zeros in FET Op Amps | 1265 |
| 18.5.3 | Bipolar Amplifier Compensation | 1266 |
| 18.5.4 | Slew Rate of the Operational Amplifier | 1266 |
| 18.5.5 | Relationships Between Slew Rate and Gain-Bandwidth Product | 1268 |
| 18.6 | High-Frequency Oscillators | 1277 |
| 18.6.1 | The Colpitts Oscillator | 1278 |
| 18.6.2 | The Hartley Oscillator | 1279 |
| 18.6.3 | Amplitude Stabilization in LC Oscillators | 1280 |
| 18.6.4 | Negative Resistance in Oscillators | 1280 |

| | | |
|--------|---------------------------|------|
| 18.6.5 | Negative G_M Oscillator | 1281 |
| 18.6.6 | Crystal Oscillators | 1283 |
| | <i>Summary</i> | 1287 |
| | <i>Key Terms</i> | 1289 |
| | <i>References</i> | 1289 |
| | <i>Problems</i> | 1289 |

APPENDICES

| | | |
|---|--|------|
| A | Standard Discrete Component Values | 1300 |
| B | Solid-State Device Models and SPICE Simulation Parameters | 1303 |
| C | Two-Port Review | 1310 |

| | |
|-------|------|
| Index | 1313 |
|-------|------|