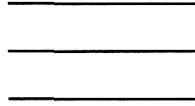


# POWER ELECTRONICS: Converters, Applications, and Design



## **NED MOHAN**

Department of Electrical Engineering  
University of Minnesota  
Minneapolis, Minnesota

## **TORE M. UNDELAND**

Department of Electrical Engineering and Computer Science  
Norwegian Institute of Technology  
Trondheim, Norway

## **WILLIAM P. ROBBINS**

Department of Electrical Engineering  
University of Minnesota  
Minneapolis, Minnesota



WILEY

**JOHN WILEY & SONS**

New York Chichester Brisbane Toronto Singapore

# CONTENTS

## PART 1 INTRODUCTION

### Chapter 1 Power Electronic Systems

1-1	Introduction	3
1-2	Scope and Applications of Power Electronics	5
1-3	Classification of Power Electronic Converters	5
1-4	About the Text	5

### Chapter 2 Overview of Power Semiconductor Switches

2-1	Introduction	7
2-2	Diodes	8
2-3	Thyristors	9
2-4	Desired Characteristics in Controllable Switches	11
2-5	Bipolar Junction Transistors (BJTs) and Monolithic Darlingtons (MDs)	15
2-6	Metal-Oxide-Semiconductor Field Effect Transistors (MOSFETs)	16
2-7	Gate-Turn-Off Thyristors (GTOs)	17
2-8	Insulated Gate Bipolar Transistors (IGBTs)	19
2-9	Comparison of Controllable Switches	19
2-10	Drive and Snubber Circuits	20
2-11	Justification for Using Idealized Device Characteristics	20
2-12	Summary	21
2-13	References	22

## PART 2 GENERIC POWER ELECTRONIC CONVERTERS

### Chapter 3 Line-Frequency Diode Rectifiers: 60 Hz ac → Uncontrolled dc

3-1	Introduction	25
3-2	Basic Rectifier Concepts	26
3-3	Single-Phase Diode Bridge Rectifiers	27
3-4	Voltage Doubler (Single-Phase) Rectifiers	33
3-5	Three-Phase Full-Bridge Rectifiers	33
3-6	Comparison of Single-Phase and Three-Phase Rectifiers	38
3-7	Inrush Current and Overvoltages at Turn-On	38
3-8	Concerns and Remedies for Input-Current Harmonics and Poor Power Factor	39
3-9	Summary	39
3-10	References	40

### Chapter 4 Line-Frequency Phase-Controlled Rectifiers and Inverters: 60 Hz ac ↔ Controlled dc

4-1	Introduction	41
4-2	Control of Line-Frequency Controlled Rectifiers and Inverters	42
4-3	Three-Phase Converter Analysis with $L_s = 0$	45
4-4	Effect of AC-Side Inductance $L_s$	47
4-5	Effect of Discontinuous Current	51
4-6	Inverter Operation	51
4-7	AC-Side Waveforms	55
4-8	Other Three-Phase Converters	61
4-9	Summary	61
4-10	References	62

### Chapter 5 DC-to-DC Switch-Mode Converters

5-1	Introduction	63
5-2	Control of dc–dc Converters	64
5-3	Step-Down (Buck) Converter	66
5-4	Step-Up (Boost) Converter	75
5-5	Buck-Boost Converter	81
5-6	Cúk dc–dc Converter	87
5-7	Full-Bridge dc–dc Converter	91
5-8	DC–DC Converter Comparison	98
5-9	Summary	100
5-10	References	101

### Chapter 6 Switch-Mode DC-to-AC Inverters: dc ↔ Sinusoidal ac

6-1	Introduction	102
6-2	Basic Concepts of Switch-Mode Inverters	104

6-3	Single-Phase Inverters	114
6-4	Three-Phase Inverters	129
6-5	Effect of Blanking Time on Output Voltage in PWM Inverters	141
6-6	Other Inverter Switching Schemes	144
6-7	Rectifier Mode of Operation	148
6-8	Summary	150
6-9	References	152

## **Chapter 7 Resonant Converters: Zero-Voltage and /or Zero-Current Switchings**

7-1	Introduction	154
7-2	Classification of Resonant Converters	156
7-3	Basic Resonant Circuit Concepts	158
7-4	Load-Resonant Converters	163
7-5	Resonant-Switch Converters	179
7-6	Zero-Voltage-Switching, Clamped-Voltage (ZVS-CV) Topologies	186
7-7	Resonant DC-Link Inverters with Zero-Voltage Switchings	193
7-8	High Frequency Link Integral-Half-Cycle Converters	195
7-9	Summary	197
7-10	References	200

## **PART 3 POWER SUPPLY APPLICATIONS**

### **Chapter 8 Switching DC Power Supplies**

8-1	Introduction	207
8-2	Linear Power Supplies	207
8-3	Overview of Switching Power Supplies	209
8-4	DC-DC Converters with Electrical Isolation	211
8-5	Control of Switch-Mode DC Power Supplies	229
8-6	Power Supply Protection	249
8-7	Electrical Isolation in the Feedback Loop	252
8-8	Designing to Meet the Power Supply Specifications	255
8-9	Summary	257
8-10	References	260

### **Chapter 9 Power Conditioners and Uninterruptible Power Supplies**

9-1	Introduction	262
9-2	Power Line Disturbances	262
9-3	Power Conditioners	265
9-4	Uninterruptible Power Supplies (UPS)	266
9-5	Summary	271
9-6	References	272

## PART 4 MOTOR DRIVE APPLICATIONS

### Chapter 10 Introduction to Motor Drives

10-1	Introduction	275
10-2	Criteria for Selecting Drive Components	277
10-3	Summary	284
10-4	References	285

### Chapter 11 DC-Motor Drives

11-1	Introduction	286
11-2	Equivalent Circuit of DC Motors	286
11-3	Permanent-Magnet DC Motors	289
11-4	DC Motors with a Separately Excited Field Winding	290
11-5	Effect of Armature Current Waveform	292
11-6	DC Servo Drives	292
11-7	Adjustable-Speed DC Drives	301
11-8	Summary	306
11-9	References	308

### Chapter 12 Induction Motor Drives

12-1	Introduction	309
12-2	Basic Principles of Induction Motor Operation	310
12-3	Induction Motor Characteristics at Rated (Line) Frequency and Rated Voltage	315
12-4	Speed Control By Varying Stator Frequency and Voltage	317
12-5	Impact of Nonsinusoidal Excitation on Induction Motors	326
12-6	Variable-Frequency Converter Classifications	329
12-7	Variable-Frequency PWM-VSI Drives	330
12-8	Variable-Frequency Square-Wave-VSI Drives	336
12-9	Variable-Frequency Current-Source Inverter (CSI) Drives	338
12-10	Comparison of Variable Frequency Drives	339
12-11	Line-Frequency Variable-Voltage Drives	339
12-12	Reduced Voltage Starting (“Soft Start”) of Induction Motors	342
12-13	Speed Control by Static Slip-Power Recovery	342
12-14	Summary	343
12-15	References	346

### Chapter 13 Synchronous-Motor Drives

13-1	Introduction	347
13-2	Basic Principles of Synchronous Motor Operation	347
13-3	Synchronous Servomotor Drives with Sinusoidal Waveforms	351
13-4	Synchronous Motor Drives with Trapezoidal Waveforms	353

13-5	Load-Commutated-Inverter (LCI) Drives	354
13-6	Cycloconverters	358
13-7	Summary	358
13-8	References	359

## **Chapter 14 Step-Motor Drives**

14-1	Introduction	361
14-2	Variable-Reluctance Step Motors	361
14-3	Permanent-Magnet Step-Motors	363
14-4	Hybrid Step-Motors	364
14-5	Modes of Excitation in Step-Motors	366
14-6	Drive Circuits for Step-Motors	370
14-7	Open-Loop Operation of Step-Motors	372
14-8	Closed-Loop Control of Step-Motors	373
14-9	Switched-Reluctance Motor Drives	373
14-10	Summary	373
14-11	References	374

## **PART 5 OTHER APPLICATIONS**

### **Chapter 15 Residential and Industrial Applications**

15-1	Introduction	377
15-2	Residential Applications	377
15-3	Industrial Applications	381
15-4	Summary	385
15-5	References	385

### **Chapter 16 Electric Utility Applications**

16-1	Introduction	386
16-2	High-Voltage DC (HVDC) Transmission	386
16-3	Static Var Control (SVC)	397
16-4	Interconnection of Renewable Energy Sources and Energy Storage	402
16-5	Summary	406
16-6	References	407

### **Chapter 17 Optimizing the Utility Interface with Power Electronic System**

17-1	Introduction	409
17-2	Generation of Current Harmonics	410
17-3	Current Harmonics and Power Factor	411
17-4	Harmonic Standards and Recommend Practices	411

17-5	Need for Improved Utility Interface	414
17-6	Improved Single-Phase Utility Interface	414
17-7	Improved Three-Phase Utility Interface	425
17-8	Electromagnetic Interference (EMI)	427
17-9	Summary	429
17-10	References	430

## **PART 6 SEMICONDUCTOR DEVICES AND CONVERTER DESIGN**

### **Chapter 18 Basic Semiconductor Physics**

18-1	Introduction	435
18-2	Conduction Processes in Semiconductors	436
18-3	PN Junctions	442
18-4	Charge Control Description of PN Junction Operation	446
18-5	Impact Ionization	448
18-6	Summary	449
18-7	References	450

### **Chapter 19 Power Diodes**

19-1	Introduction	451
19-2	Basic Structure and I-V Characteristics	451
19-3	Breakdown Voltage Considerations	453
19-4	On-State Losses	459
19-5	Switching Characteristics	462
19-6	Schottky Diodes	467
19-7	Diode Snubbers	470
19-8	Summary	478
19-9	References	479

### **Chapter 20 BJTs with Drive and Snubber Circuits**

20-1	Introduction	480
20-2	Vertical Power Transistor Structures	480
20-3	I-V Characteristics	482
20-4	Physics of BJT Operation	484
20-5	Switching Characteristics	490
20-6	Breakdown Voltages	497
20-7	Second Breakdown	498
20-8	On-State Losses	500
20-9	Safe Operating Areas	501
20-10	Design of Drive Circuits for BJTs	503
20-11	Snubber Circuits for BJTs and Darlingtons	520
20-12	Summary	532
20-13	References	534

**Chapter 21 Power MOSFETs**

21-1	Introduction	535
21-2	Basic Structure	535
21-3	I-V Characteristics	538
21-4	Physics of Device Operation	540
21-5	Switching Characteristics	545
21-6	Operating Limitations and Safe Operating Areas	550
21-7	Design of Gate Drive Circuits	559
21-8	Snubber Circuits	565
21-9	Summary	566
21-10	References	567

**Chapter 22 Thyristors**

22-1	Introduction	568
22-2	Basic Structure	568
22-3	I-V Characteristics	570
22-4	Physics of Device Operation	571
22-5	Switching Characteristics	575
22-6	Methods of Improving $dI/dt$ and $dV/dt$ Ratings	581
22-7	Thyristor Gating Circuits	583
22-8	Snubber Circuits for Thyristors	587
22-9	Summary	590
22-10	References	592

**Chapter 23 Gate Turn-Off Thyristors**

23-1	Introduction	593
23-2	Basic Structure and I-V Characteristics	593
23-3	Physics of Turn-Off Operation	595
23-4	GTO Switching Characteristics	597
23-5	Snubber Circuits	603
23-6	Overcurrent Protection of GTOs	604
23-7	Summary	605
23-8	References	606

**Chapter 24 Insulated Gate Bipolar Transistors**

24-1	Introduction	607
24-2	Basic Structure	607
24-3	I-V Characteristics	610
24-4	Physics of Device Operation	610
24-5	Latchup in IGBTs	613
24-6	Switching Characteristics	615
24-7	Device Limits and Safe Operating Areas	618
24-8	Drive and Snubber Circuits	619
24-9	Summary	620
24-10	References	621



**Chapter 25 Emerging Devices and Circuits**

25-1	Introduction	622
25-2	Power Junction Field Effect Transistors	622
25-3	Field-Controlled Thyristor	627
25-4	JFET-Based Devices Versus Other Power Devices	630
25-5	MOS-Controlled Thyristors	630
25-6	High Voltage Integrated Circuits	632
25-7	New Semiconductor Materials	636
25-8	Summary	637
25-9	References	638

**Chapter 26 Passive Components and Practical Converter Design Considerations**

26-1	Introduction	639
26-2	Design of Inductors	639
26-3	Transformer Design	646
26-4	Selection of Capacitors	650
26-5	Resistors	651
26-6	Current Measurements	651
26-7	Heat sinking	653
26-8	Circuit Layout	654
26-9	Summary	655
26-10	References	656

**Index****657**