

# SENSORS AND SIGNAL CONDITIONING

---

## **RAMÓN PALLÁS-ARENY**

Department of Electronic Engineering  
Polytechnic University of Catalonia  
Barcelona, Spain

## **JOHN G. WEBSTER**

Department of Electrical and Computer Engineering  
University of Wisconsin  
Madison, Wisconsin



A Wiley-Interscience Publication

**JOHN WILEY & SONS, INC.**

New York • Chichester • Brisbane • Toronto • Singapore

# CONTENTS

## Preface

xi

## 1 Introduction to Measurement Systems

1

- 1.1 General Concepts and Terminology, 1
  - 1.1.1 Measurement systems, 1
  - 1.1.2 Transducers, sensors, and actuators, 2
  - 1.1.3 Signal conditioning and display, 4
  - 1.1.4 Interfaces, data domains, and conversion, 4
- 1.2 Sensor Classification, 6
- 1.3 General Input-output Configuration, 7
  - 1.3.1 Interference and internal perturbations, 7
  - 1.3.2 Compensation techniques, 8
- 1.4 Static Characteristics of Measurement Systems, 10
  - 1.4.1 Accuracy, precision, and sensitivity, 10
  - 1.4.2 Other characteristics: Linearity and resolution, 13
  - 1.4.3 Systematic errors, 15
  - 1.4.4 Random errors, 15
- 1.5 Dynamic Characteristics, 16
  - 1.5.1 Zero-order measurement systems, 17
  - 1.5.2 First-order measurement systems, 18
  - 1.5.3 Second-order measurement systems, 21
- 1.6 Input Characteristics: Impedance, 26
- 1.7 Primary Sensors, 28
  - 1.7.1 Temperature sensors: Bimetals, 28

- 1.7.2 Pressure sensors, 29
- 1.7.3 Flow velocity and flow-rate sensors, 32
- 1.7.4 Force and torque sensors, 38
- 1.8 Problems, 39
- References, 40

## 2 Resistive Sensors

41

- 2.1 Potentiometers, 41
- 2.2 Strain Gages, 45
  - 2.2.1 Fundamentals: Piezoresistive effect, 45
  - 2.2.2 Types and applications, 50
- 2.3 Resistive Temperature Detectors (RTDs), 52
- 2.4 Thermistors, 55
  - 2.4.1 Models, 55
  - 2.4.2 Thermistor types and applications, 61
  - 2.4.3 Linearization, 64
- 2.5 Magnetoresistors, 67
- 2.6 Light-dependent Resistors (LDRs), 68
- 2.7 Resistive Hygrometers, 72
- 2.8 Problems, 74
- References, 77

## 3 Signal Conditioning for Resistive Sensors

79

- 3.1 Measurement of Resistance, 79
- 3.2 Voltage Dividers, 82
  - 3.2.1 Potentiometers, 82
  - 3.2.2 Application to thermistors, 90
  - 3.2.3 Dynamic measurements, 92
- 3.3 Wheatstone Bridge: Balance Measurements, 92
- 3.4 Wheatstone Bridge: Deflection Measurements, 95
  - 3.4.1 Sensitivity and linearity, 95
  - 3.4.2 Analog linearization of resistive sensor bridges, 100
  - 3.4.3 Sensor bridge calibration, 101
  - 3.4.4 Difference and average measurements: Compensation, 102
  - 3.4.5 Power supply of Wheatstone bridges, 109
  - 3.4.6 Detection methods for Wheatstone bridges, 112
- 3.5 Instrumentation Amplifiers, 113
  - 3.5.1 Differential amplifiers, 113
  - 3.5.2 Instrumentation amplifiers based on two op amps, 117
  - 3.5.3 Instrumentation amplifiers based on three op amps, 118

- 3.5.4 Monolithic instrumentation amplifiers, 121
- 3.6 Interference, 123
  - 3.6.1 Interference types and reduction, 123
  - 3.6.2 Signal circuit grounding, 127
  - 3.6.3 Shield grounding, 129
  - 3.6.4 Isolation amplifiers, 134
- 3.7 Problems, 136
  - References, 139

#### **4 Reactance Variation and Electromagnetic Sensors** **140**

- 4.1 Capacitive Sensors, 140
  - 4.1.1 Variable capacitor, 140
  - 4.1.2 Differential capacitor, 150
- 4.2 Inductive Sensors, 152
  - 4.2.1 Reluctance variation sensors, 152
  - 4.2.2 Eddy current sensors, 157
  - 4.2.3 Linear variable differential transformers (LVDTs), 159
  - 4.2.4 Variable transformers: Synchros, resolvers, and Inductosyn, 166
  - 4.2.5 Magnetoelastic sensors, 179
- 4.3 Electromagnetic Sensors, 181
  - 4.3.1 Sensors based on Faraday's law, 181
  - 4.3.2 Hall effect sensors, 187
- 4.4 Problems, 191
  - References, 193

#### **5 Signal Conditioning for Reactance Variation Sensors** **195**

- 5.1 Problems and Alternatives, 195
- 5.2 AC Bridges, 198
  - 5.2.1 Sensitivity and linearity, 198
  - 5.2.2 Capacitive bridge analog linearization, 201
  - 5.2.3 AC amplifiers: Power supply decoupling, 202
  - 5.2.4 Electrostatic shields: Driven shields, 205
- 5.3 Carrier Amplifiers, 207
  - 5.3.1 Fundamentals and structure, 207
  - 5.3.2 Phase-sensitive detectors, 210
  - 5.3.3 Application to LVDTs, 215
- 5.4 Variable Oscillators, 217
  - 5.4.1 Sinusoidal oscillators, 218
  - 5.4.2 Relaxation oscillators, 222
- 5.5 Resolver-to-digital and Digital-to-resolver Converters, 223
  - 5.5.1 Synchro-to-resolver converters, 223

- 5.5.2 Digital-to-resolver converters, 226
- 5.5.3 Resolver-to-digital converters, 227
- 5.6 Problems, 229
- References, 231

**6 Generating Sensors**

**233**

- 6.1 Thermoelectric Sensors: Thermocouples, 233
  - 6.1.1 Thermoelectric effects, 233
  - 6.1.2 Common thermocouples, 237
  - 6.1.3 Practical thermocouple laws, 242
  - 6.1.4 Cold junction compensation in thermocouple circuits, 243
- 6.2 Piezoelectric Sensors, 247
  - 6.2.1 The piezoelectric effect, 247
  - 6.2.2 Piezoelectric materials, 250
  - 6.2.3 Applications, 252
- 6.3 Pyroelectric Sensors, 257
  - 6.3.1 The pyroelectric effect, 257
  - 6.3.2 Pyroelectric materials, 259
  - 6.3.3 Radiation laws: Planck, Wien, and Stefan-Boltzmann, 260
  - 6.3.4 Applications, 262
- 6.4 Photovoltaic Sensors, 263
  - 6.4.1 The photovoltaic effect, 263
  - 6.4.2 Materials and applications, 263
- 6.5 Electrochemical Sensors, 265
- 6.6 Problems, 267
- References, 269

**7 Signal Conditioning for Self-generating Sensors**

**271**

- 7.1 Chopper and Low-drift Amplifiers, 272
  - 7.1.1 Offset and drifts in op amps, 272
  - 7.1.2 Chopper amplifiers, 275
  - 7.1.3 Chopper-stabilized amplifiers, 277
  - 7.1.4 Autozero amplifiers, 278
  - 7.1.5 Offset and drifts in instrumentation amplifiers, 280
- 7.2 Electrometer Amplifiers, 281
- 7.3 Charge Amplifiers, 285
- 7.4 Noise in Amplifiers, 289
  - 7.4.1 Noise in op amps, 289
  - 7.4.2 Noise in instrumentation amplifiers, 294
- 7.5 Problems, 297
- References, 299

|  |            |
|--|------------|
| <b>8 Digital Sensors</b>                                 | <b>300</b> |
| 8.1 Position Encoders, 300                               |            |
| 8.1.1 Incremental position encoders, 301                 |            |
| 8.1.2 Absolute position encoders, 307                    |            |
| 8.2 Variable Frequency Sensors, 309                      |            |
| 8.2.1 Quartz digital thermometers, 310                   |            |
| 8.2.2 Vibrating wire strain gages, 311                   |            |
| 8.2.3 Vibrating cylinder sensors, 313                    |            |
| 8.2.4 SAW sensors, 314                                   |            |
| 8.2.5 Digital flowmeters, 316                            |            |
| 8.3 Problems, 317  |            |
| References, 317  |            |
| <b>9 Other Sensing Methods</b>                           | <b>319</b> |
| 9.1 Sensors Based on Semiconductor Junctions, 319        |            |
| 9.1.1 Thermometers based on semiconductor junctions, 320 |            |
| 9.1.2 Magnetodiodes and magnetotransistors, 324          |            |
| 9.1.3 Photodiodes and phototransistors, 325              |            |
| 9.2 Sensors Based on MOSFET Transistors, 331             |            |
| 9.3 Charge-coupled Sensors, 334                          |            |
| 9.3.1 Fundamentals, 334                                  |            |
| 9.3.2 Types of CCD imaging sensors and applications, 337 |            |
| 9.4 Ultrasonic-based Sensors, 341                        |            |
| 9.4.1 Principles, 341                                    |            |
| 9.4.2 Applications, 343                                  |            |
| 9.5 Fiber-optic Sensors, 345                             |            |
| 9.6 Problems, 348  |            |
| References, 350  |            |
| <b>10 Telemetry and Data Acquisition</b>                 | <b>352</b> |
| 10.1 Data-acquisition System Structure, 353              |            |
| 10.2 Telemetry System Structure, 355                     |            |
| 10.3 Amplitude Telemetry, 357                            |            |
| 10.3.1 Voltage telemetry, 357                            |            |
| 10.3.2 Current telemetry, 359                            |            |
| 10.4 Frequency Telemetry, 365                            |            |
| 10.4.1 Voltage-to-frequency converters, 366              |            |
| 10.4.2 Frequency-to-voltage converters, 369              |            |
| 10.5 Multiplexing Systems, 371                           |            |
| 10.5.1 Frequency-division multiplexing, 371              |            |
| 10.5.2 Time-division multiplexing, 374                   |            |

10.6 Problems, 378  
References, 379

|  |            |
|--|------------|
| <b>General Bibliography</b>            | <b>380</b> |
| <b>Appendix: Solutions to Problems</b> | <b>386</b> |
| <b>Index</b>                           | <b>395</b> |